

ELECTRICAL MACHINES LAB NOTES

AKSHANSH CHAUDHARY

Electrical Machines Lab Notes, First Edition

Copyright © 2013 Akshansh

ALL RIGHTS RESERVED.

Presented by: Akshansh Chaudhary
Graduate of BITS Pilani, Dubai Campus
Batch of 2011

Course content by: Dr. R. Gomathi Bhavani
Then Faculty, BITS Pilani, Dubai Campus

Layout design by: AC Creations © 2013



The course content was prepared during Fall, 2012.

More content available at: www.Akshansh.weebly.com


DISCLAIMER: While the document has attempted to make the information as accurate as possible, the information on this document is for personal and/or educational use only and is provided in good faith without any express or implied warranty. There is no guarantee given as to the accuracy or currency of any individual items. The document does not accept responsibility for any loss or damage occasioned by use of the information contained and acknowledges credit of author(s) where ever due. While the document makes every effort to ensure the availability and integrity of its resources, it cannot guarantee that these will always be available, and/or free of any defects, including viruses. Users should take this into account when accessing the resources. All access and use is at the risk of the user and owner reserves that right to control or deny access.

Information, notes, models, graph etc. provided about subjects, topics, units, courses and any other similar arrangements for course/paper, are an expression to facilitate ease of learning and dissemination of views/personal understanding and as such they are not to be taken as a firm offer or undertaking. The document reserves the right to discontinue or vary such subjects, topic, units, courses, or arrangements at any time without notice and to impose limitations on accessibility in any course.

8 Expt 1 : No load Test on single ϕ transformer.

- ✓ OC test :- Circuit diagram - OC - HY side
SC Test :- " - SC LV side
- ✓ OC Test :- Set rated voltage using variac $\rightarrow 115 V$
- ✓ SC Test - Set rated current " " $\rightarrow 434 A (1000 \text{ m}A / 220 V)$

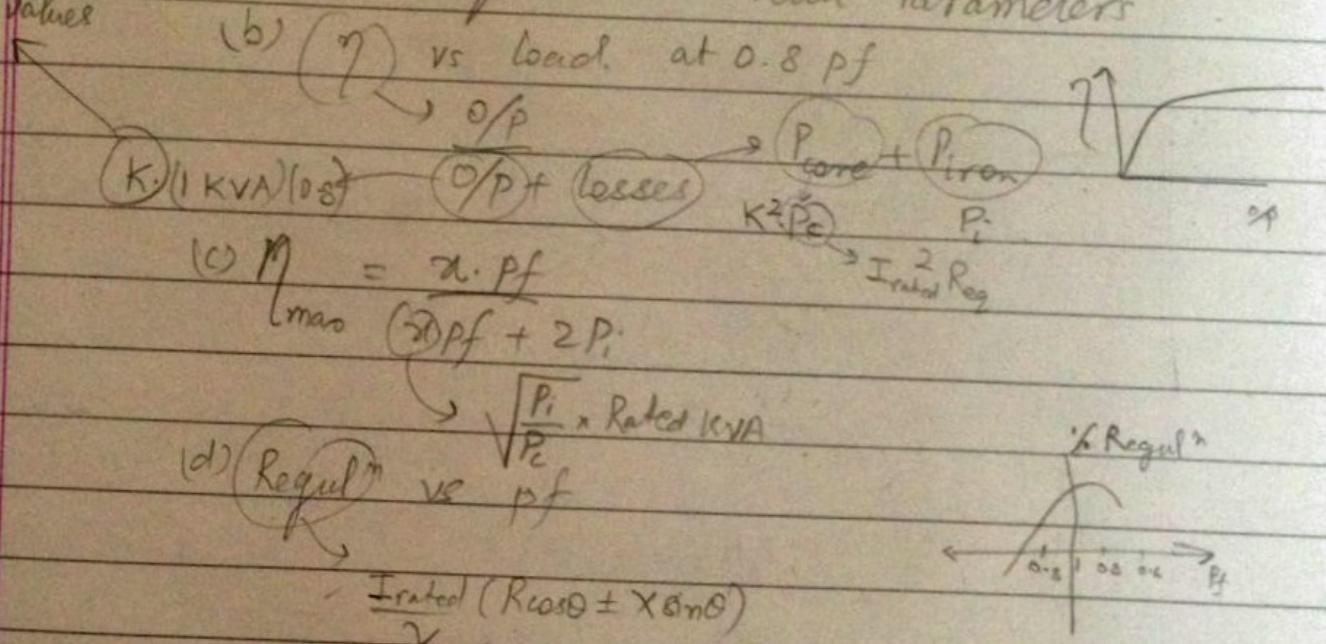load values (a) Find equivalent circuit Parameters



8 Expt 2 : No load test on DC Shunt motor.

Find Reg

(a) Find η vs o/p \rightarrow Gen \rightarrow Motor

(b) Field control & Arm. control

(a)

$$\eta = \frac{O/P}{O/P + \text{losses}} \rightarrow VI_L$$

by $O/P + \text{losses}$

$$VI_L$$

$$\eta_m = \frac{i/P}{i/P} - \text{losses}$$

$$I_{LD} = I_{Av} + I_f$$

S1 : Vary R_a ext to bring to

220 V

S2 : Vary ER to bring to

1500 rpm.

I_{Av}, I_f ✓

$$P_L = P_K + P_V \rightarrow I_{av}^2 R_a$$

$$\sqrt{I_{LD}^2} - I_{av}^2 R_a = 16.8 A$$

(b) Field control

$V = 220$ (Keep const)

Vary FR $\rightarrow n$

I_f




Arm. control.

$I_f = \text{constt}$ (any value)

Vary $R_{a\text{ ext}}$

n

V_a

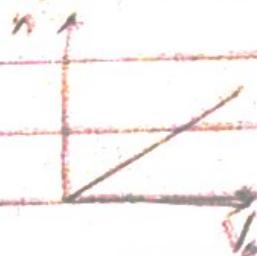

Q Expt. 3 : No load test on synchronous machine

Find freq

(a) Plot $V_{o\text{cl}}$ vs I_f

- OC Test
- S1) Vary FR to bring $n_c = 1500 \text{ rpm}$
 - S2) $\uparrow I_f$ & note V
 - Vary $R_{a\text{ ext}}$ I_f
 - $V_{o\text{cl}} = (V_{ph} - V_{o\text{cl}})/\sqrt{3}$

(b) Plot I_{sc} vs I_f

S1) Switch off armature ($R_{a\text{ ext}}$) excitn

S2) Put S1 on

S3) Switch on $R_{a\text{ ext}}$ excitn

S4) Vary $R_{a\text{ ext}}$ to $\uparrow I_f$ & note I_{sc}


I_f

I_{sc}

\rightarrow Any of nonlinear line

(c) Z_s (unsaturated) = $V_{o\text{cl}}/\sqrt{3}$

I_{sc}

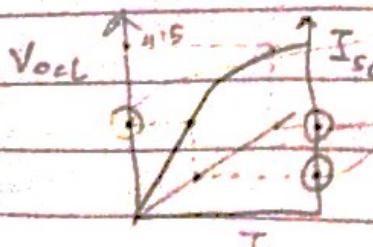

(d) Z_s (adj) = $415/\sqrt{3}$

(e) Z_s vs I_f graph

using Partial table

Ex-4 (rated for SG)

$$(f) V_{regul^n} = \frac{V}{I} (R_{load} + (X \sin \theta))$$

$$V = 415 \text{ (Rated for SG)}$$

$$R_{eq} \rightarrow \sqrt{Z_{adj}^2 - R_{eq}^2}$$


Expt 4: No load test on DC Shunt Generator

Find R_{eq} (a) Plot E_a vs I_f


S1) Vary FR to set to rated speed (1500 rpm)

S2) Vary R_{load} to get values of E_a & I_f

S3) Plot graph

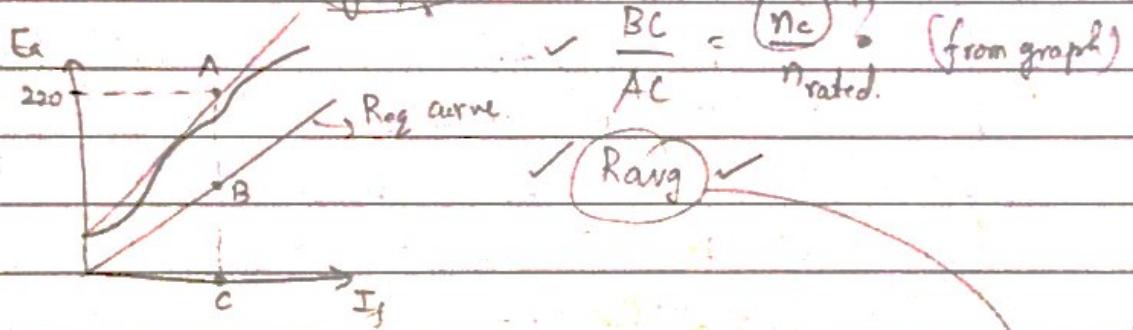(b) Plot E_a vs n

S1) Vary FR to set to 1500 rpm

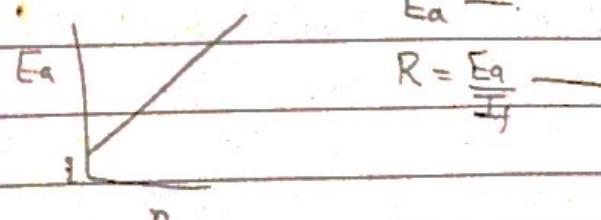S2) Note value of $I_f \rightarrow 220 \rightarrow R_s$ S3) Vary R_{load} $\rightarrow n = \frac{E_a}{I_f}$ 

8

Expt 10 - No load test on Induction Motor

Find R_2

{ S1) Set 415 V using variac

{ S2) Note:- I_{OL} , $W (= P_{OL})$ ($V_L = 415$)Block rotor test.

S1) Block rotor

S2) Set Variac s.t $I_{BRL} (= I_{OL}) = 4.8 A$ Note:- V_{BRL} , $W (= P_{BRL})$

8

Expt 9 - Load test on 3 ϕ Induction MotorS1) Vary variac to bring $V_m = 415 V$.S2) Vary (FR)_g & set $V_g = 220 V$.

S3) Take reading at No load.

S4) Switch on load & take readings of I_p , $W (= P_{in})$, n Block rotor

S1) Bring variac to zero

S2) Block rotor

S3) Again set it s.t $V_m = 415 V$. & Vary (FR)_g to $V_g = 220 V$ S4) Note value of P_{BR} (from wattmeter)

$$(a) \eta = \frac{P_o}{P_{in}} \rightarrow (P_{in} - P_{BR}) / 0.995 = P_{BR} + (P_{con} \#)$$

$$(b) \eta f = \frac{P_{in}}{\sqrt{3} V_i I_2}$$

$$(c) T = \frac{P_o}{2\pi n/60}$$

$$(d) \text{Slip} = \frac{n_s - n}{n_s} \times 1000$$

Initially, $(FR)_m = \text{min}$

$(FR)_g = \text{max}$

Expt 5

Puffin

Date _____
Page _____

Load Test on DC Shunt Generator

(a) V_L vs I_L


s1) $(FR)_m$ set to 1500 rpm

s2) $(FR)_g$ set to $V_{rated} = 220 V$

s3) connect load & \uparrow step by step.

Note - V_L & I_L in each case

↓ Larger end
near Loadings
point

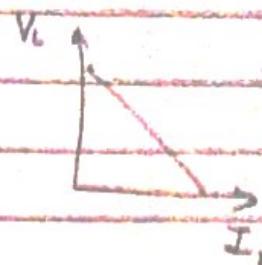

Expt 6(i)

Sumner's Test

(a) Find Parameters of equivalent circuit of transformer

(single ϕ)

s1) Variac 1 \rightarrow Set to $V_{rated} = 115 V$

s2) Check $V_3 (= 0)$ \rightarrow else reverse HV₁ terminals

s3) Close switch. Vary Variac 2 \rightarrow Rated current (4.34 A)

(LV) $V_1, I_1 (= 2I_o), W_1 (= 2P_i)$

(HV) $V_2 (= V_{sc}), I_2 (= I_{sc}), W_2 (= 2P_{sc})$

$$a = 2(1230/115)$$

Expt 6(ii)

Scott Connection


(a) Find η on diff't loads

s1) Vary Variac to set Secondary voltage to 115 V

So, Primary is automatically set to 230 V

s2) Apply diff't loads & find $\eta = \frac{\text{op}}{\text{i/p}} = \frac{V_A I_a + V_B I_b}{W_1 + W_2}$

Graph η vs op.

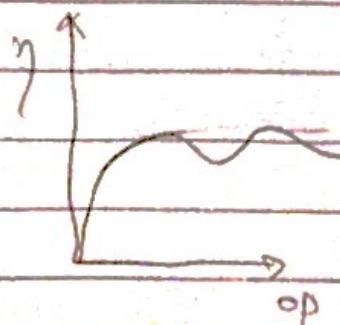

Expt 7: Hopkinson's Test

Find P_{req}

$$P_{req} = R_{arm} \\ = R_{ag}$$


- S1) Adjust $(FR)_m$ to bring to rated speed (1500 rpm)
- S2) Adjust $(FR)_g$ to make $V_2 = 0$
- S3) Close switch.
- S4) keeps changing $(FR)_m$ & $(FR)_g$, 4-5 times to keep η const (1500). Note values of $I_{am}, I_{fm}, I_{ag}, I_{fg}$

Finding η_m & η_g

Armature + field + Stray


$$I_{am}^2 R_{arm} + V I_{fm} + P_s \rightarrow \frac{1}{2} (P_{in(m)} - P_a)$$

P_s

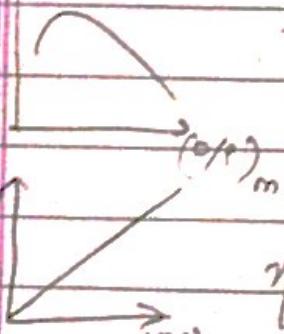

$$\eta_m = \frac{\% \text{-loss}}{i/p} = \frac{V(I_{fm} + I_{am}) - \text{Loss}}{V(I_{fm} + I_{am})}$$

$$I_{am}^2 R_{arm} + I_{fm}^2 R_f$$

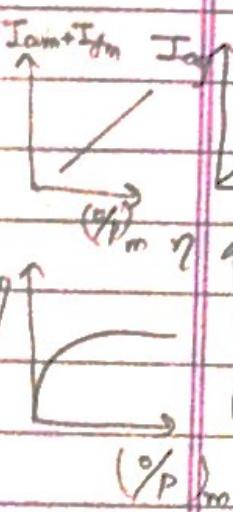

$$\eta_g = \frac{\% \text{-loss}}{c/p} \rightarrow V I_{ag}$$

Arm + field + Stray

$$I_{ag}^2 R_{ag} + V I_{fg} + P_s$$

$$\frac{1}{2} (P_{in(gm)} - P_a)$$

$$V(I_{ag} - I_{fg}) \quad I_{ag}^2 R_{ag} + I_{fg}^2 R_f$$

Expt 8:

Load Test on Sync. Machine (Motor)

Part ①


- S1) Turn on DC

S2) Vary FR to set to $\eta_{rated} = 1500$ rpm

S3) Vary R_{agent} to set to 400 V (See box)

- S4) Red button Turn on

beside machine
beside bus

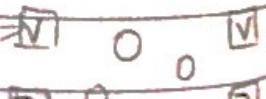


- S5) Turn on AC


S6) Note phase (connected to RYB & see 5 or 2 dir w)

S7) Vary R_{agent} to bring $\eta = 50$ Hz

S8) Vary FR to make bulb off

S9) Switch on Load

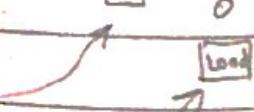

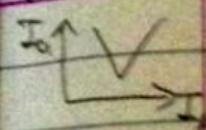

Part ②) Add load from loading unit & vary R_{out} for +ve & -ve values of I_f



- ✓ P_{in} (Wattmeter)
 - ✓ I_a
- } Bring it back to lower value of I_f before Part ③

Part ③

Block rotor : Sync. motor :

s1) Switch off DC supply

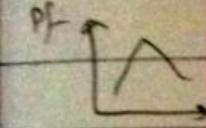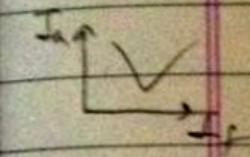s2) Vary R_{out} & note Readings of P_{in} , I_a for +ve & -ve values of I_f



$$I_f / P_f = \frac{P_{in}}{\sqrt{3} V_L I_L}$$

$$\frac{V}{\sqrt{3} V_L I_L} \rightarrow \begin{aligned} I_a - I_f &: \text{Gen} \\ I_a + I_f &: \text{Motor} \end{aligned}$$

