

ELECTICAL MACHINES NOTES

AKSHANSH CHAUDHARY

Electrical Machines Notes, First Edition

Copyright © 2013 Akshansh

ALL RIGHTS RESERVED.

Presented by: Akshansh Chaudhary
Graduate of BITS Pilani, Dubai Campus
Batch of 2011

Course content by: Dr. R. Gomathi Bhavani
Then Faculty, BITS Pilani, Dubai Campus

Layout design by: AC Creations © 2013



The course content was prepared during Fall, 2012.

More content available at: www.Akshansh.weebly.com

DISCLAIMER: While the document has attempted to make the information as accurate as possible, the information on this document is for personal and/or educational use only and is provided in good faith without any express or implied warranty. There is no guarantee given as to the accuracy or currency of any individual items. The document does not accept responsibility for any loss or damage occasioned by use of the information contained and acknowledges credit of author(s) where ever due. While the document makes every effort to ensure the availability and integrity of its resources, it cannot guarantee that these will always be available, and/or free of any defects, including viruses. Users should take this into account when accessing the resources. All access and use is at the risk of the user and owner reserves that right to control or deny access.

Information, notes, models, graph etc. provided about subjects, topics, units, courses and any other similar arrangements for course/paper, are an expression to facilitate ease of learning and dissemination of views/personal understanding and as such they are not to be taken as a firm offer or undertaking. The document reserves the right to discontinue or vary such subjects, topic, units, courses, or arrangements at any time without notice and to impose limitations on accessibility in any course.

TRANSFORMERS

* Flux:


- Mutual: Flux linked to both windings of transformer.
- Leakage: Flux linked to only one windings of transformer.

• Limbs of a transformer: The 2 sides where coil is wound.

• LV & HV winding: Low Voltage & High Voltage winding.

↳ LV winding close to the core & ~~is~~ $\frac{1}{2}$ of HV windings ~~close~~ above LV. (all insulated). This is CORE TYPE (To maximise mutual flux & reduce Leakage flux).

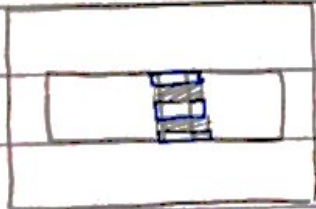• SHELL TYPE (Sandwich winding): 3 limbs \exists . Winding along central limb. LV & HV are cut & placed alternatively.



* In terms of μ of operⁿ:-

1. Iron core: 25 - 400 Hz.

2. Air core: High μ operⁿ.

* In terms of cooling:

1. Naturally cooled (small rated transformers)

2. Forced cooling transformer (big transformer in cooling oil)

* Transformer tanks (with cooling oil) are SEALED.
Why? : To prevent moisture ingress.

* Cooling oil : prevents heat (due to resistance) protect insulⁿ.

* Transformer is a static device.
↳ Its efficiency will be higher than rotating machines. (friction, air drag)

* Primary & Secondary windings are isolated from each other & the core.

◦ CORE TYPE : concentric coils

◦ SHELL TYPE : sandwich or pancake coils.

* Windings are of solid/stranded Cu or Al strip conductors.

Impo Insulation class : A, B, C, F, H.

↳ Highly inflammable ^{industry} insulⁿ : class H insulⁿ.

◦ Class A can withstand upto 105°C

◦ " H " " " 180°C

* Natural Cooling

◦ Small size transformers - Natural circulⁿ

- because of large coeff. of expansion of oil
- Heat removed from walls of the tank by radiation or air convection.

- Cooling area of tank increased by cooling fins or tubes - Medium size transformers.

* Forced Cooling

◦ For size > 5mVA, supplementing tank surface by a separate radiator in which oil is circulated

by a pump.

- Better cooling options - oil to air heat exchanger, oil to water exchanger.
- Formⁿ of hot spots in conditioner damages core or insulⁿ property - ducts inside core/winding to remove heat are cut.

* Transformer oil : highly refined mineral oil
: Canola oil can be used.

* Oil : cools transformer
: provides insulⁿ.

* Superconducting windings : Removes Cu loss

* When transformer is on NO-LOAD, it's open circuited. So, no current should flow in secondary. Only current (I_0) flows in the primary called as EXCITING CURRENT or NO-LOAD CURRENT.

* EME eqⁿ of a transformer :-

Derivⁿ

N_1 : no. of turns of primary

N_2 : " " " secondary


ϕ_m : max. flux in core (Wb)

f : frequency of A.C i/p (Hz)

Avg rate of flux = $\frac{\phi_m}{\frac{1}{4f}}$ = $4f\phi_m$ Wb/s.

★ $\phi_{max} = \frac{V}{\sqrt{2} \pi f N}$ Wb → *max core flux in each winding under no load*

Puffin
Date _____
Page _____

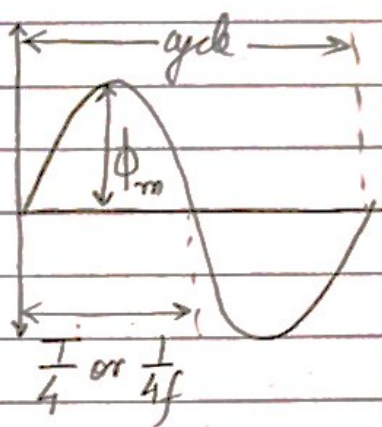

Rate of change of flux/turn = induced emf
Avg. induced emf/turn = $4f \phi_m$ volt

For sinusoidal flux, rms value = Avg value x Form factor
RMS value of emf/turn = $1.11 \times 4f \phi_m = 4.44 f \phi_m$ volt

RMS value of emf in whole of primary (E) = $4.44 f \phi_m \times N_1$

Assuming no leakage flux & no winding resistances
 $E_1 \approx V_1$ & $e_2 = N_2 \frac{d\phi}{dt}$

With secondary open, $V_2 = e_2 \Rightarrow \frac{E_1}{E_2} = \frac{N_1}{N_2} = a$

$$\left[\frac{E_1}{E_2} = \frac{N_1}{N_2} = a \text{ (ratio of turns)} \right]$$

or Transfer Ratio
or Voltage Ratio

* For a transformer

$$V_1 I_1 = V_2 I_2$$

$$\Rightarrow \frac{V_1}{V_2} = \frac{I_2}{I_1} = \frac{a_T}{4} = \frac{1}{4f}$$

★ Ideal Transformer :-

Assumptions :-

1. Primary & Secondary have no winding resistance (no loss in R)
2. No leakage flux (all flux confined to core & link both windings)
3. Core has infinite permeability (so that no I_m (magnetising current) is needed for given ϕ_{max} ($\phi_m = \frac{NI}{\mu}$) \rightarrow MMF
4. $I_i = 0$ i.e. core loss = 0. \rightarrow Permeability
 $\frac{v_1}{v_2} = \frac{E_1}{E_2} = \frac{N_1}{N_2} = a$


★ IDEAL TRANSFORMER ON LOAD

$i_2 \neq 0$; secondary mmf $\mathcal{F}_2 = i_2 N_2$ opposes core flux (Lenz Law)

To keep $\phi = \text{const.}$, i_1 from primary flows (\because Resistance winding = 0)

To mmf balance:
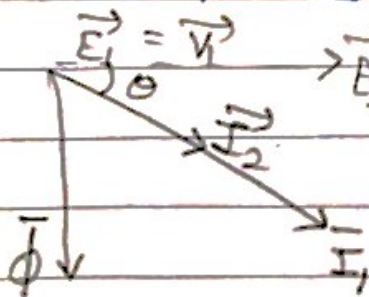
$$i_1 N_1 = i_2 N_2 \Rightarrow \frac{i_1}{i_2} = \frac{N_2}{N_1} = \frac{1}{a}$$




$$P_1 = v_1 i_1 = v_2 i_2 = P_2$$

\Rightarrow Instt. Power of Primary =

\Rightarrow Instt. Power of Secondary
 \Rightarrow no loss in ideal transformer.

★ Impedance: Resistance offered in AC circuit.

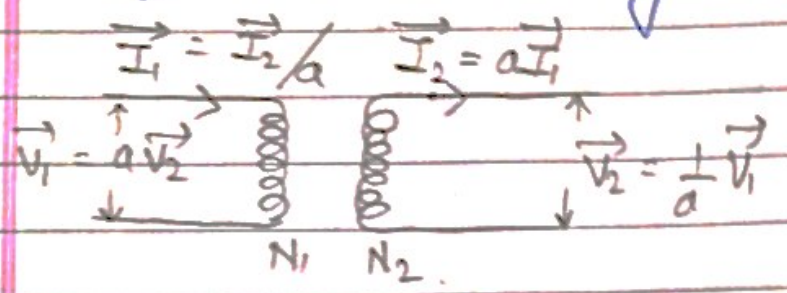• equivalent circuit diagram for ideal transformer.



$V_2 = Z_2 I_2$
 $\Rightarrow \left(\frac{N_2}{N_1} \right) V_1 = Z_2 I_1$
 $\Rightarrow \frac{V_1}{I_1} = \left(\frac{N_1}{N_2} \right)^2 Z_2 = Z_1'$

$\frac{V_1}{V_2} = \frac{N_1}{N_2}$ & $\frac{I_1}{I_2} = \frac{N_2}{N_1}$

$\Rightarrow \frac{V_1 / V_2}{N_1 / N_2} = \frac{I_1 / I_2}{N_2 / N_1} \Rightarrow \frac{V_1}{I_1} = \left(\frac{N_1}{N_2} \right)^2 Z_2 \quad \triangleright a^2$

$\frac{V_2}{I_2} = \left(\frac{N_1}{N_2} \right)^2 Z_2$

$\Rightarrow Z_1 = \left(\frac{N_1}{N_2} \right)^2 Z_2 = a^2 Z_2 = Z_2'$

= Impedance of secondary referred to the primary as seen by

So, $Z_1' = \frac{1}{a^2} Z_1$ (||ly)

$Y_2' = \frac{1}{a^2} Y_2$ (admittance)

★ RULES

1. Secondary impedance referred to primary as seen by

$Z = a^2 Z_2$

; a = ratio of transformⁿ.

* $\frac{1}{\text{Resistance (R)} \Omega} = \text{Conductance (G)} \Omega^{-1}$ * $\frac{1}{\text{Impedance (Z)} \Omega} = \text{Admittance (Y)} \Omega^{-1}$

* $\frac{1}{\text{Reactance (X)} \Omega} = \text{Susceptance (B)} \Omega^{-1}$

2. Primary impedance referred to secondary

$$= \frac{1}{a^2} Z_1$$

3. Secondary admittance referred to primary

$$= \frac{1}{a^2} Y_2$$

4. Primary admittance referred to secondary

$$= a^2 Y_1$$

* a. Transferring resistance from secondary to primary

$$R_2' = a^2 R_2$$

(b) ~~Seco~~ Primary resistance referred to secondary

$$R_1' = \frac{1}{a^2} R_1$$

* Leakage flux is modelled as reactance (X)
 ↳ Reactance comes through leakage flux

* R (Resistance), X (Reactance), B_m (magnetic susceptance), G_i (Iron loss conductance).

All in one circuit


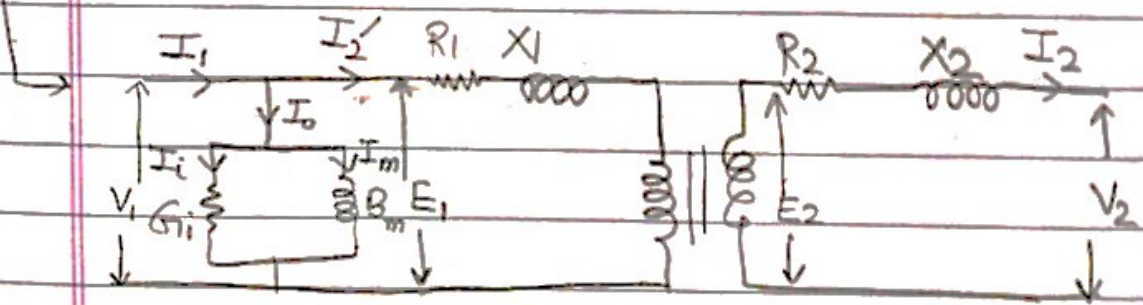


fig: 3.14


* Secondary voltage: also called Terminal voltage.

* No load phasor diagram:

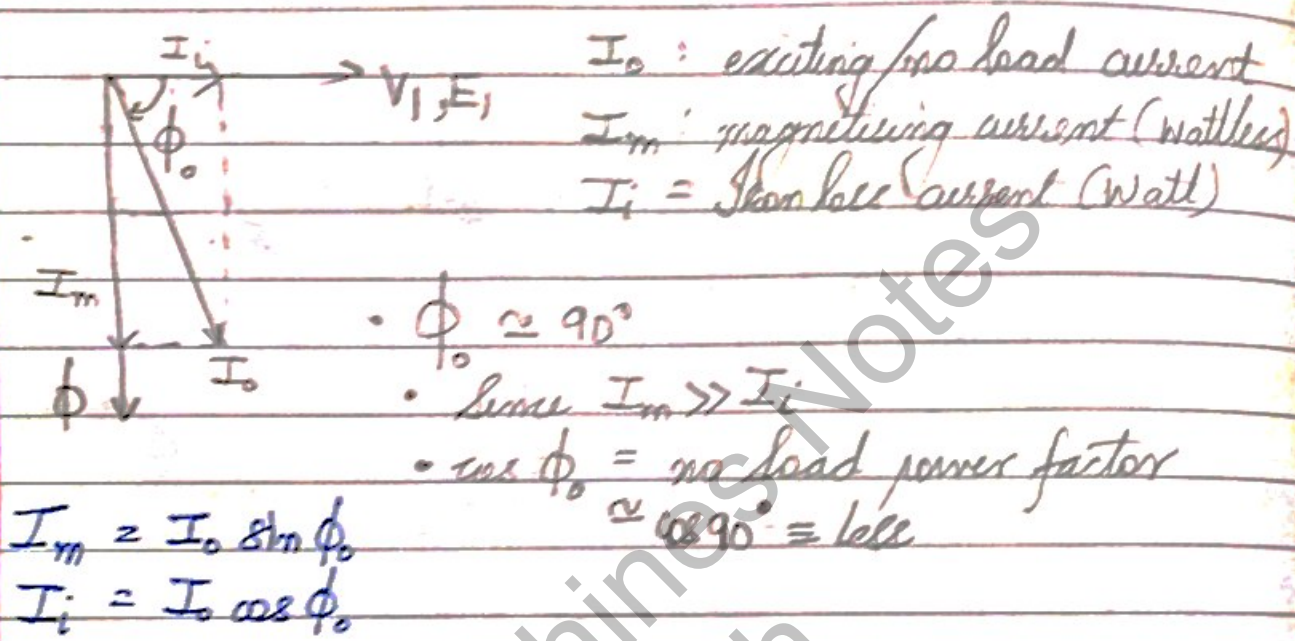

* Power transformer approximate form of T circuit model.

Phasor diagram

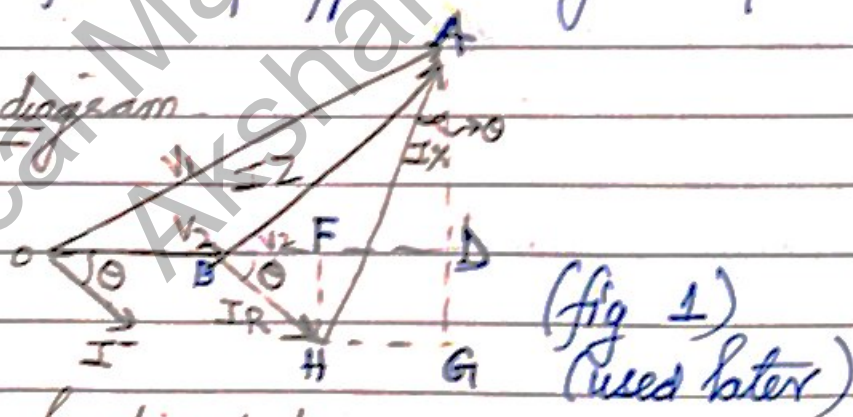

→ non loading test

* TESTING OF TRANSFORMER


OC, SC test

Sumpner's test

R, I, S → P
 25 S → P
 10 a?
 1/2

OC test

SC test

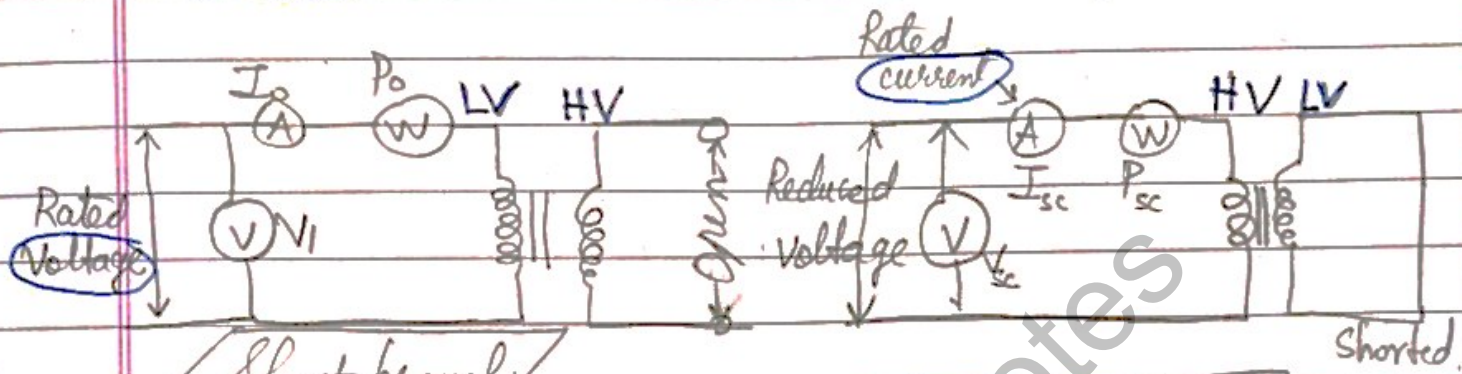

Shunt branch parameters:

$$Y_0 \text{ or } G_0 = \frac{I_0}{V_1} \quad \text{Core loss} = P_0$$

w.r.t
 LV side

$$G_i = \frac{P_0}{V_1^2}$$

$$B_m = \sqrt{\frac{V_1^2}{V_1^2} - G_i^2}$$

Series Parameters:

$$Z = \frac{V_{sc}}{I_{sc}}$$

$$R = \frac{P_{sc}}{I_{sc}^2}$$

$$X = \sqrt{Z^2 - R^2}$$

w.r.t
 HV side.
 (So we can change from R to R' & all)

- In OC test, wattmeter is a measure of iron core loss.

Full load copper loss = P_{sc}

Wattmeter in SC test is a measure of full load copper loss (Proportional to I^2)

Copper loss

↳ Full load = 1000 W, say

↳ 1/2 load

$$= \left(\frac{1}{2}\right)^2 \times 1000$$

(not $\frac{1}{2} \times 1000$)

Q Obtain the approximate equivalent circuit of a given
 LV \leftarrow $\overset{\text{HV}}{200/6000}$ V, 30 KVA single phase transformer having
 the following test results:

OC Test: $V_1 = 200$ V
 $I_0 = 6.2$ A
 $P_0 = 360$ W } on LV side

(See fig
 on previous
 page)

SC Test: $V_{sc} = 75$ V
 $I_{sc} = 18$ A
 $P_{sc} = 600$ W } on HV side

Ans: - OC Test (LV side)

$$Y_0 = \frac{6.2}{200} = 31 \times 10^{-3} \text{ } \Omega^{-1}$$

$$G_0 = \frac{360}{4 \times 10^4} = 9 \times 10^{-3} \text{ } \Omega^{-1}$$

$$B_m = \sqrt{(31)^2 - 9^2} \times 10^{-3}$$

$$= \sqrt{880} \times 10^{-3}$$

$$B_m = 29.664 \times 10^{-3} \text{ } \Omega^{-1}$$

SC Test (HV side)

$$Z = \frac{75}{18} = 4.166 \text{ } \Omega$$

$$R = \frac{600}{18^2} = 1.85185 \text{ } \Omega$$

$$X = \sqrt{(4.166)^2 - (1.85)^2} = 3.731783 \text{ } \Omega$$

31

900

961

81

880

2

2 | 880

245

105

648

101

849

89

4

480

Now, transform R & X to LV side (as we got them in HV)


$$R' = a^2 R$$

$$X' = a^2 X$$

LV side

$$R' = 18.5 \text{ m}\Omega$$

$$X' = 37.3 \text{ m}\Omega$$

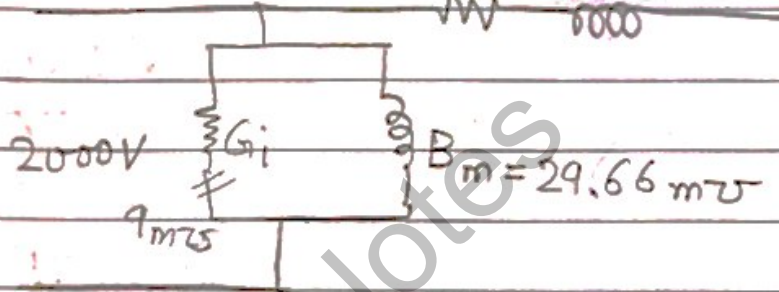


$$a = \frac{V_1}{V_2} = \frac{200}{2000}$$

$$\Rightarrow a = \left(\frac{1}{10}\right)$$

HV side

$$R' = 18.5 \text{ m}\Omega$$

$$X' = 37.3 \text{ m}\Omega$$

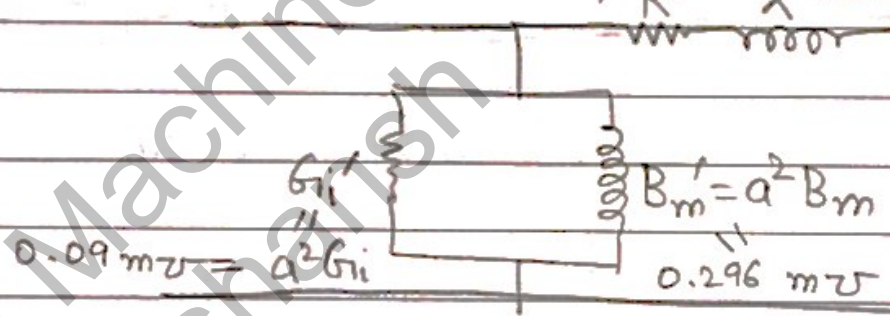

$$\ast \text{ Efficiency } (\eta) = \frac{\text{O/P}}{\text{I/P}}$$

→ max. efficiency when $Cu \text{ loss} = Fe \text{ loss}$
 → of corresponding to η_{max} , $I_2 = \sqrt{\frac{W_i}{R_{02}}}$

• R_{01} : equivalent resistance in the primary

$$= R_1 + R'_2$$

$$= R_1 + a^2 R_2 ; a = \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{i_2}{i_1}$$

$$V_2 I_2 \cos \theta_2$$

$$\eta = \frac{\text{O/P}}{\text{O/P} + \text{losses}} = \frac{\text{I/P} - \text{losses}}{\text{I/P}}$$

$$\rightarrow I^2 R + P_i$$


* Full load Cu loss = $I_2^2 R_{02}$
 $= I_1^2 R_{01}$
 $= I_1^2 R_1 + I_2^2 R_2$

Primary i/p = $V_1 I_1 \cos \phi_1$
 $\eta = \frac{V_1 I_1 \cos \phi_1 - \text{Losses}}{V_1 I_1 \cos \phi_1}$
 $= \frac{V_1 I_1 \cos \phi_1 - I_1^2 R_{01} - W_i}{V_1 I_1 \cos \phi_1}$
 $= 1 - \frac{I_1 R_{01}}{V_1 \cos \phi_1} - \frac{W_i}{V_1 I_1 \cos \phi_1}$

• Differentiating w.r.t I_1 , $\frac{d\eta}{dI_1} = 0 \Rightarrow W_i = I_1^2 R_{01}$
 So, for max η , Cu loss = Iron loss
 \rightarrow o/p current corresponding to η_{max} , $I_2 = \sqrt{\frac{W_i}{R_{02}}}$

* SUMPNER'S TEST or Back to Back Test

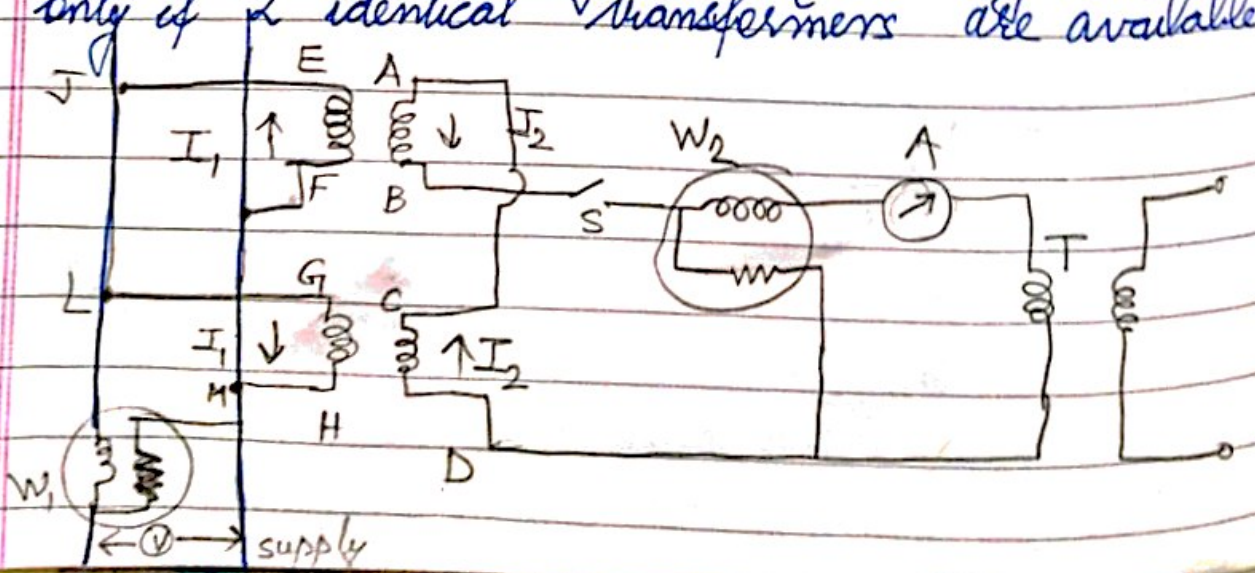
• Sumpner's test for regulⁿ, η , heating under load only if 2 identical transformers are available.



- Primaries of transformers are connected in parallel across the same AC supply.
- With switch S open, $W_1 =$ core loss for 2 transformers
- Secondaries of 2 transformers so connected that their potentials are in ϕ opposⁿ to each other (i.e. If $V_{AB} = V_{CD}$ & A is joined to C while B is to D.)
- T is auxiliary low voltage transformer, which is used to circulate full load current (or any desired current) in secondary circuit after closing switch S.
- I_2 flows from D to C & then from A to B.
- W_2 reads full load Cu loss (or Cu loss at I_2)
- Net power i/p = $2P_0 + 2P_c =$ only losses.



VOLTAGE REGULATION

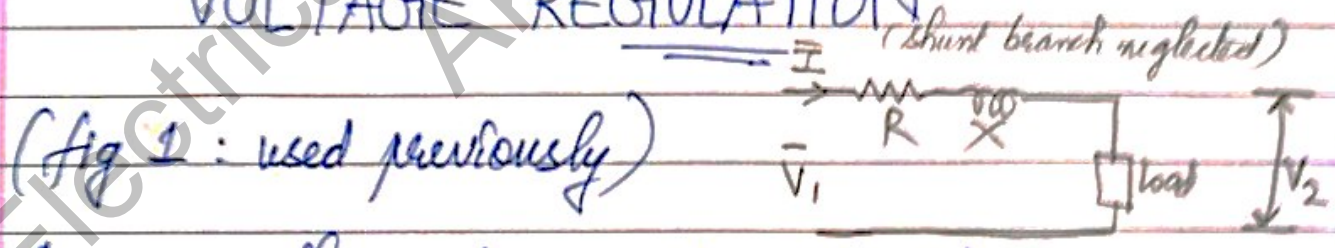

Approp. voltage drop ; $V_1 = OA = OD$
 $V_1 - V_2 = BD = BF + FD = BF + HG$
 $= IR \cos \phi + IX \sin \phi$
 $= I(R \cos \phi + X \sin \phi)$; ϕ lagging
 $= I(R \cos \phi - X \sin \phi)$; ϕ leading
 \Rightarrow Voltage regulⁿ = $\frac{I(R \cos \phi \pm X \sin \phi)}{V_2} \times 100$.

$$\left(\frac{\begin{matrix} \text{Secondary vol. on no load} \\ - \text{Secondary vol. on full load} \end{matrix}}{\text{Secondary vol. on full load}} \times 100 \right)$$

• For max. regulⁿ; $\frac{d(\text{Reg})}{d\theta} = 0 = -R \sin\theta + X \cos\theta$

$$\text{So, } \tan\theta = \frac{X}{R}$$

Power factor

$$\text{Pf} = \cos\theta = \frac{R}{\sqrt{R^2 + X^2}}; \text{ lagging}$$

$$\text{Hly, Pf} = \cos\theta = \frac{X}{\sqrt{R^2 + X^2}}; \text{ leading}$$

• all inductive loads : lagging power factor
 capacitive loads : leading power factor
 resistive loads : Unity power factor (UPF)

Q. A 50 kVA, 1100/220 V, 50 Hz, 1 phase (ϕ) transformer has
 $R_1 = 0.125 \Omega$ $X_1 = 0.625 \Omega$
 $R_2 = 0.005 \Omega$ $X_2 = 0.025 \Omega$

Find equivalent circuit w.r.t HV side
 LV side

Core loss = 580 W

Find η at (i) full load ^{unity} power factor

(ii) $\frac{3}{4}$ full load, 0.8 power factor lagging

$$a = \frac{1100}{220} = 5$$

w.r.t HV

$$\left. \begin{aligned} R_{01} &= \text{Equivalent resistance at primary} = R_1 + R_2' \\ &= R_1 + a^2 R_2 \\ &= 0.25 \end{aligned} \right\}$$

$$\left. \begin{array}{l} \text{w.r.t} \\ \text{HV} \end{array} \right\} X_{01} = X_1 + 0^2 X_2 = 1.25$$

$$R_{02} = R_2 + \frac{1}{0^2} R_1 = 0.01$$

$$\left. \begin{array}{l} \text{w.r.t} \\ \text{LV} \end{array} \right\} X_{02} = X_2 + \frac{1}{0^2} X_1 = 0.05$$

(i) Full load current (Secondary) $I_2 = \frac{50000 \text{ VA}}{220 \text{ V}}$

$$= 227.27 \text{ A}$$

$$\text{Full load Cu loss} = I_2^2 R_{02}$$

$$= 516.516529$$

$$\text{Total loss} = \text{Iron loss} + \text{Full load Cu loss}$$

$$\text{Full load o/p} = \text{Full load kVA} \times \text{power factor}$$

$$= 50,000 \times 1$$

$$= 50,000 \text{ W}$$

(a) $\eta = \frac{\text{o/p}}{\text{o/p} + \text{losses}}$

$$= \frac{50,000}{50,000 + 580 + 516.5} = 0.9785402$$

$$= 97.854\%$$

(b) f.l. o/p = f.l. kVA \times pf

$$= \frac{3}{4} (50,000) \times 0.8$$

$$= \frac{4}{4} (40,000) \frac{3}{4} = 30000$$

$$\eta = \frac{30000}{30000 + 580 + \left[\frac{516.5 \times 3}{4} \right] \times 100}$$

$$= 0.971800$$

$$= 97.18\%$$

\rightarrow Cu loss changes

\rightarrow Iron loss doesn't change

Q, The above transformer is fully loaded on secondary side at (a) 0.8 power factor lagging
(b) 0.8 pf leading
(c) unity pf

while it is fed on primary side at 1100 V

Calculate %age regulⁿ & voltage at secondary terminals for above condⁿ

(a) Total voltage drop at secondary ^{at fl} at 0.8 pf lag

$$= I_2 (R_{02} \cos \phi + X_{02} \sin \phi)$$

$$= 227.27 [(0.01 \times 0.8) + (0.05 \times 0.6)]$$

$$= 8.636 \text{ V}$$

$$\% \text{age regul}^n = \frac{8.63}{220} \times 100 = 3.925 \%$$

Secondary voltage at fl at 0.8 pf lag

$$= 211.37$$

(b) Leading

$$\text{Total} = I_2 (R_{02} \cos \phi - X_{02} \sin \phi)$$

$$= -4.99994 \text{ V}$$

$$\% \text{age regul}^n = -2.2727 \%$$

Secondary voltage at f.l at 0.8 pf lead

$$= 220.5 (-4.99)$$

$$= 224.9999 \text{ V}$$

(c) Unity

$$\text{Total} = I_2 (R_{02} (1) + X_{02} (0)) \\ = 2.2727$$

$$\% \text{age regul}^n = 1.03\%$$

Secondary voltage at fl. at unity pf

$$= 220 - 2.2727$$

$$= 220 - 2.2727 \text{ V}$$


★ pf
Lagging
Leading
upf

% regulation

+ve ✓ always true

-ve * may/may not be true

+ve ✓ always true

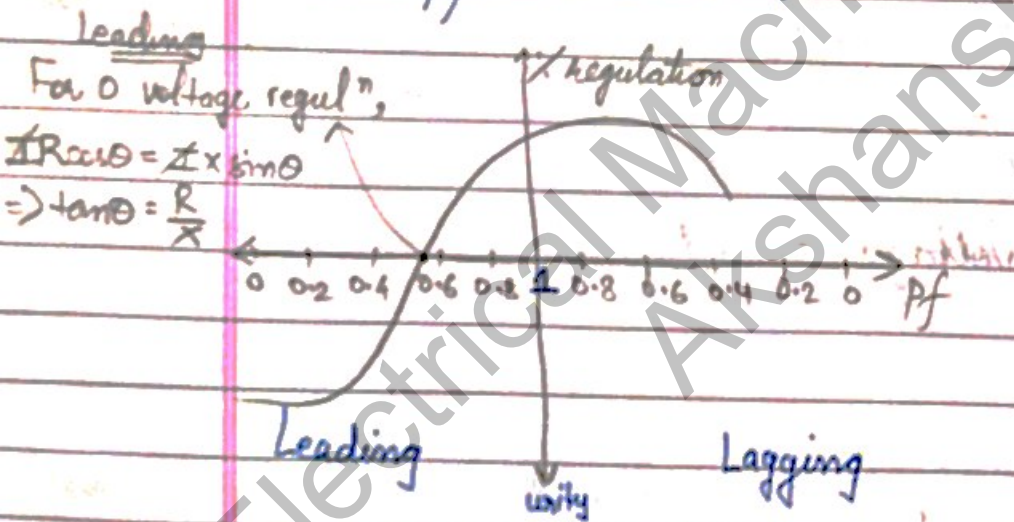

Q 9.11 The following test results were obtained on
20 kVA, 2200/220V transformer

OC Test (LV): 220V, 1.1A, 125W $\rightarrow W_i$

SC Test (HV): 52.7V, 8.4A, 287W

(a) upf load on secondary, with $V_2 = 220 \text{ V}$, $\eta = ?$

(b) Transformer is fully loaded. Determine $\cos \theta$ load
pf for zero voltage regulⁿ.

$$\Rightarrow \text{leading } \tan^{-1} \left(\frac{R}{X} \right) = \theta$$

- * DC Test gives Iron loss.
- * SC Test gives full load Cu loss.

$$a = \frac{2200}{220} = 10$$

$$R_{01} = \frac{287}{(8.4)^2} = 4.0674 \Omega$$

$$X_{01} = \sqrt{Z^2 - R^2} = 4.775645 \Omega$$

$$Z_{01} = \frac{52.7}{8.4} = 6.273 \Omega$$

For max η ; $I_1^2 R_{01} = \text{Iron loss} = 125 \text{ W } (W_i)$

$$\Rightarrow I_1 = \sqrt{\frac{125}{4.0674}}$$

$$\Rightarrow I_1 = 5.5436 \text{ A}$$

Current corresponding to η_{max}

$$\begin{aligned} \text{o/p} &= VI \cos \phi \\ &= (2200)(5.5436) \quad (1) \\ &= 12188 \text{ W} \end{aligned}$$

$$\eta = \frac{\text{o/p}}{\text{o/p} + \text{losses}}$$

Same as Iron loss \rightarrow 125
 Core loss + Iron loss \rightarrow 125

$$= 0.9799$$

$$\Rightarrow \eta_{\text{max}} = 97.99\%$$

SC Test

Rated current : $\frac{20 \text{ KVA}}{2200} = \frac{20,000}{2200} = 9.09 \text{ A } (\neq 8.4 \text{ A})$


Full load Cu loss = $\frac{287}{(8.4)^2} \times (9.09)^2$ (P \propto I²)

THREE-PHASE TRANSFORMERS

- γ : Wye, star
- Δ : Delta


\rightarrow phase
 3 ϕ transformer : A set of 3 similar single phase transformers may be connected to form a 3 phase transformer.

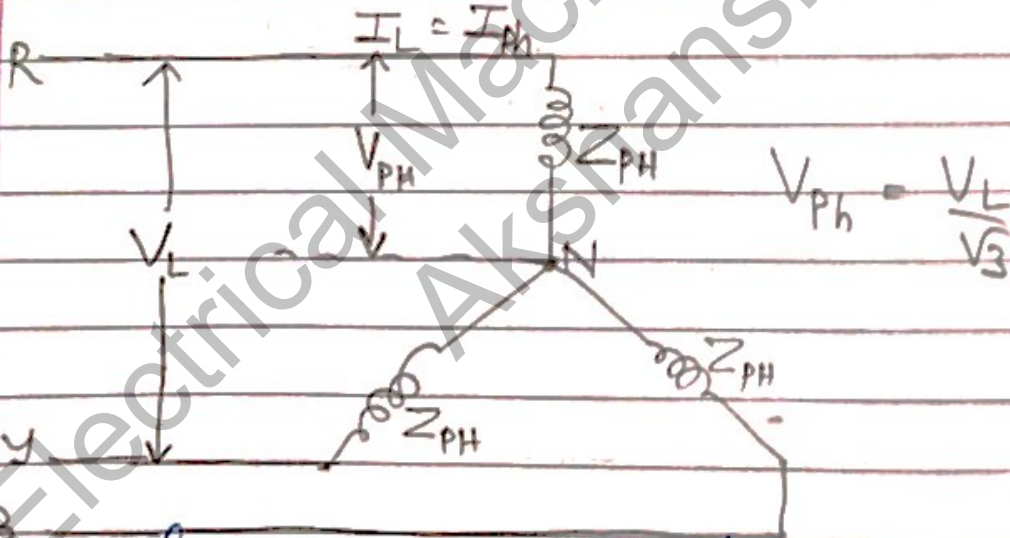In a balanced 3 phase star connected system, phase voltage (V_{ph}) = $\frac{\text{line voltage } (V_L)}{\sqrt{3}}$



And line current (I_L) = Phase current (I_{ph})

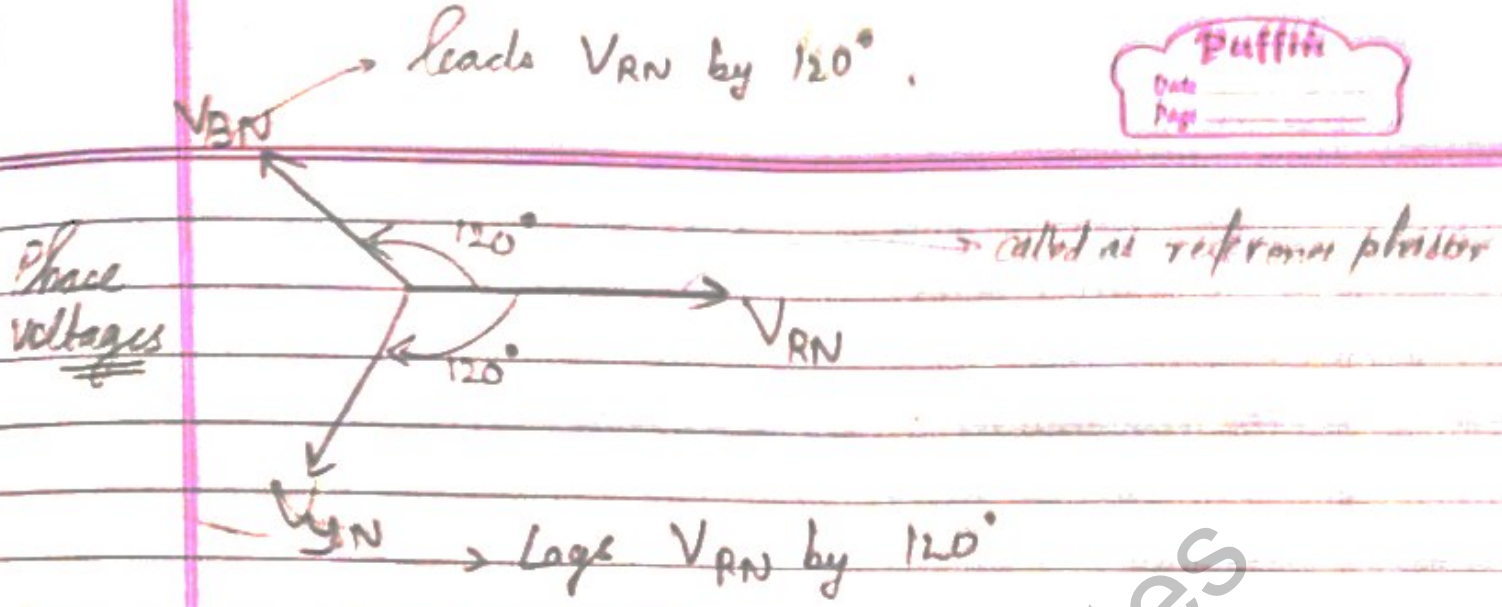
- Above, \exists 3 line voltages $V_{(R \text{ to } Y)}$, $V_{(Y \text{ to } B)}$, $V_{(R \text{ to } B)}$
- Line voltage : Also called line to line voltage
- Phase impedance : Also called per phase impedance
- Above, \exists 3 phase voltages: V_{RN} , V_{YN} , V_{BN}
 or, can be said V_R , V_Y , V_B



* Line voltages also have a phase shift of 120° between them.

Delta Connected Sys.

• 3 line voltages V_{RY}, V_{YB}, V_{BR}

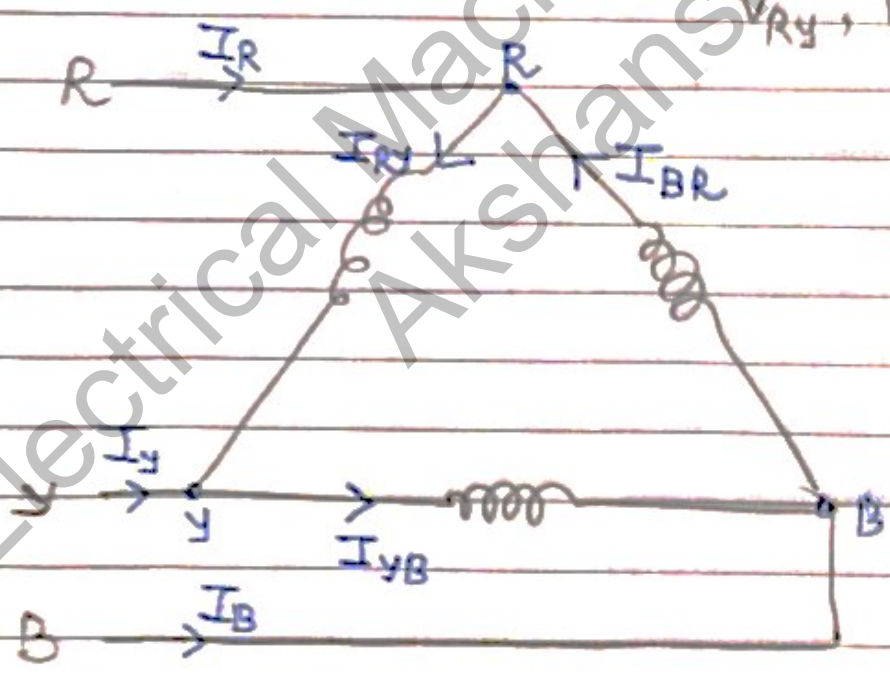


For delta connection :- $V_L = V_{ph}$.

$I_{ph} = \frac{1}{\sqrt{3}} I_L$

* Notation :- Upper case : PRIMARY ; lower case : SECONDARY

- $+30^\circ$ connection :- Wye-Delta connected transformer.
Phase shift of 30° b/w V_{AN} & V_{ab}
- -30° connection :- Delta-Wye connected transformer.
Phase shift of -30° b/w V_{AB} & V_{an} .

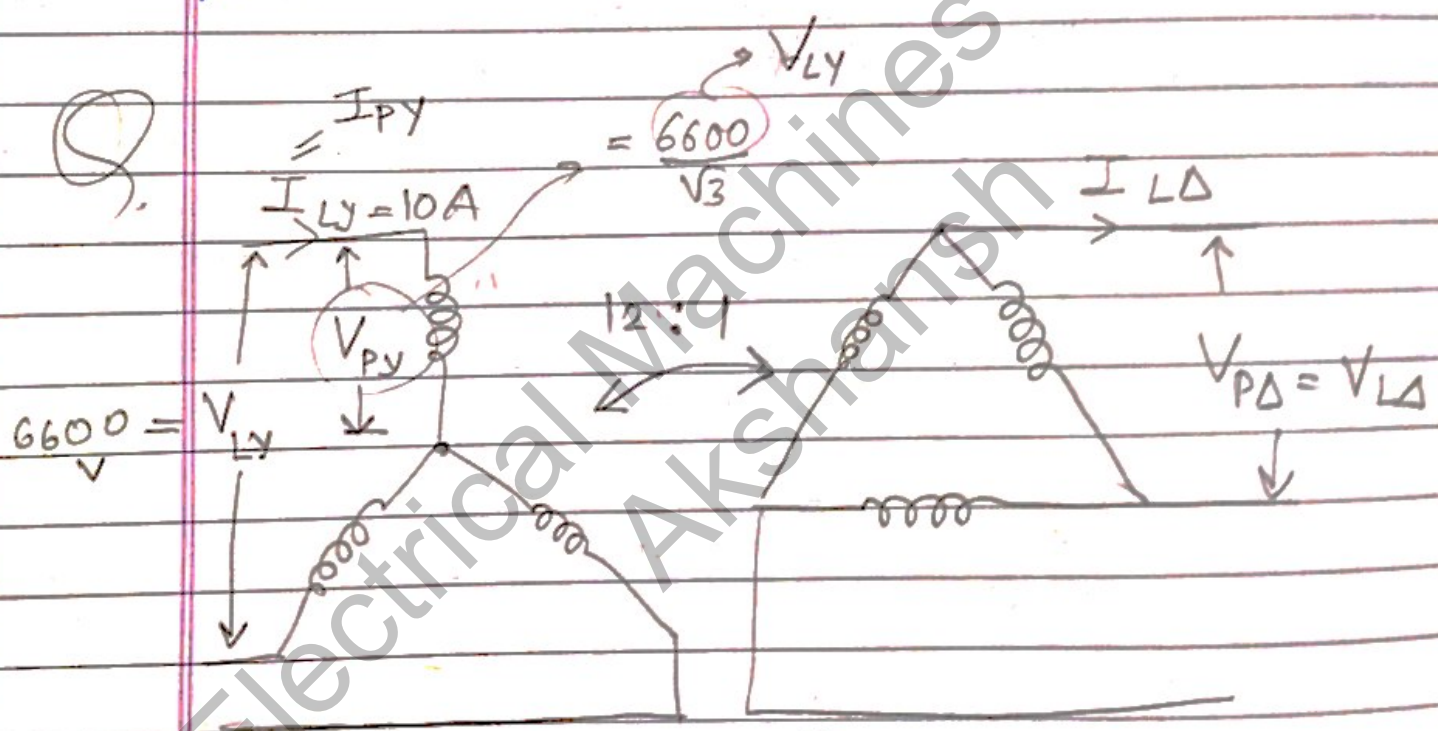Imp * Transfer ratio / transformⁿ ratio is the ratio b/w the phase values.



Find $V_{L\Delta} = ?$ $I_{L\Delta} = ?$

O/P KVA = ?

$$\left(\begin{aligned} &= \sqrt{3} V_{L\Delta} I_{L\Delta} \text{ : formula} \\ &= 3 V_{P\Delta} I_{P\Delta} \end{aligned} \right)$$

- P: Phase
- L: Line
- Y: Wye \equiv Star
- Δ : Delta.

Transformation Ratio is :-

$$\frac{\text{Primary}}{\text{Secondary}} \leftarrow \frac{V_{PY}}{V_{PD}} = \frac{I_{PD}}{I_{PY}}$$



Here, $\frac{V_{PY}}{V_{PD}} = 12$; $\frac{I_{PD}}{I_{PY}} = 12$

$I_{PY} (= I_{LY})$

Also, $V_{PY} = \frac{V_{LY}}{\sqrt{3}} = \frac{6600}{\sqrt{3}} = 3810.62 \text{ V}$

So, $V_{PD} = V_{LD}$, $I_{PD} = \frac{I_{LD}}{\sqrt{3}}$

$12 \times I_{PY} = 12 \times 10$

$\Rightarrow I_{LD} = \sqrt{3} \times 10 \times 12 \text{ A} = 207.84$

$\frac{V_{PY}}{V_{LD}} = 12 \Rightarrow V_{LD} = \frac{V_{PY}}{12} = \frac{V_{LY}}{\sqrt{3} \times 12} = \frac{6600}{12 \times \sqrt{3}}$


$= 317.55 \text{ V}$

O/P KVA = $\frac{\sqrt{3} \times 6600}{12 \times \sqrt{3}} \times \frac{\sqrt{3} \times 10 \times 12}{\sqrt{3}} \text{ KVA}$

$= 114315.35 \text{ VA}$

$= 114.315 \text{ KVA}$

Ans

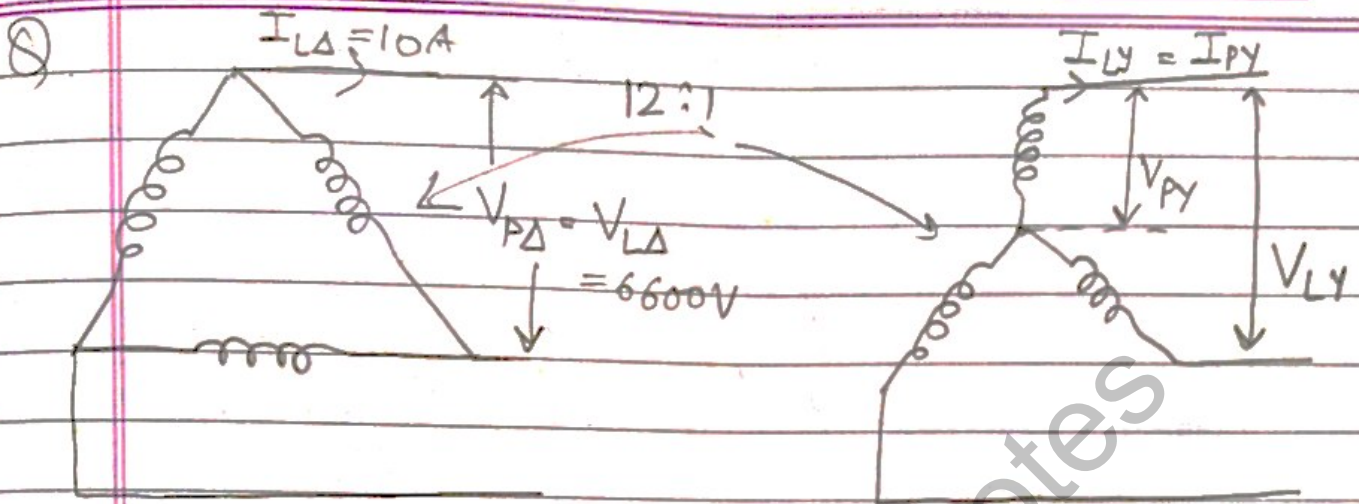

Find:- $V_{LY} = ?$, $I_{LY} = ?$ o/p KVA = ?
 $(= \sqrt{3} V_{L\Delta} I_{L\Delta})$
 $(= 3 V_{P\Delta} I_{P\Delta})$

Transformⁿ ratio = 12 = $\frac{V_{P\Delta}}{V_{PY}} = \frac{I_{PY}}{I_{P\Delta}}$

$\therefore V_{PY} = \frac{V_{P\Delta}}{12} = \frac{6600}{12}$

$\checkmark V_{LY} = \sqrt{3} V_{PY} = \frac{\sqrt{3}}{12} \times 6600 = 952.62\text{V}$

$12 = \frac{I_{PY}}{I_{P\Delta}} = \frac{I_{LY}}{I_{P\Delta}}$

$\Rightarrow I_{LY} = 12 \times I_{P\Delta}$

$I_{L\Delta} = \sqrt{3} I_{P\Delta}$

$\Rightarrow I_{P\Delta} = \frac{10}{\sqrt{3}}$

$\checkmark \Rightarrow I_{LY} = \frac{12 \times 10}{\sqrt{3}} = 69.284\text{A}$

\checkmark o/p KVA = $\sqrt{3} \times 6600 \times 10 = 114312\text{VA}$
 $= 114.312\text{KVA}$

Q The HV terminals of a 3 phase bank of 3 single phase transformers are connected to a 3 wire, 3 phase, 11 KV line-to-line sys.

The LV terminals are connected to a 3 wire 3 phase load, rated of 1000 KVA & 2200 V line-to-line. Specify the voltage, current & KVA ratings of each transformer (both HV & LV windings) for following cond^{ns}:

(a) HV \rightarrow Y ; LV \rightarrow Δ

(b) HV \rightarrow Δ ; LV \rightarrow Y

(c) HV \rightarrow Y ; LV \rightarrow Y

(d) HV \rightarrow Δ ; LV \rightarrow Δ

Given:-

$$V_{HV} = 11 \text{ KV}, \quad V_{LV} = 2200 \text{ V}$$

For Y side :- $V_{LY} = V_{PY}$

For Δ side :- $V_{LA} = V_{PA}$

(a) Transformⁿ ratio = $\frac{11/\sqrt{3}}{2.2} \left(\frac{V_{PY}}{V_{PA}} \right) = \frac{I_{PA}}{I_{PY}}$

$$V_{PY} = 11/\sqrt{3} \text{ KV}$$

$$V_{PA} = 2.2 \text{ KV}$$

$$V_{LY} = 11 \text{ KV}$$

$$V_{LA} = 2.2 \text{ KV}$$

$$\left. \begin{array}{l} I_{PY} = \\ I_{LY} = \end{array} \right\} \text{equal}$$

$$I_{PA} = 454.54$$

$$I_{LA} = 262.439$$

$$157.454$$

$$\text{Transfer ratio} = \frac{I_{PA}}{I_{PY}} = \frac{11}{\sqrt{3} \times 2.2}$$

$$\begin{aligned} \text{OP KVA} &= \sqrt{3} \times V_{LA} \times I_{LA} \\ \Rightarrow 1000 &= \sqrt{3} \times 2.2 \times I_{LA} \end{aligned}$$

$$\Rightarrow I_{LA} = \frac{1000}{\sqrt{3} \times 2.2} = 262.489 \text{ A}$$

$$I_{PB} = \sqrt{3} I_{LA} = \frac{1000}{2.2} \text{ A}$$

$$\Rightarrow I_{PY} = \sqrt{3} \times 2.2 \times I_{PA}$$

$$\Rightarrow I_{PY} = \frac{11}{\sqrt{3} \times 2.2} \times \frac{1000}{2.2} =$$

$$\begin{aligned} \text{(b) Transform ratio} &= \frac{V_{PA}}{V_{PY}} = \frac{I_{PY}}{I_{PA}} \\ &= \frac{11}{2.2/\sqrt{3}} = \frac{I_{PY}}{I_{PA}} \quad \text{--- (1)} \end{aligned}$$

V_{PY}	V_{PA}
V_{LY}	V_{LA}
I_{PY}	I_{PA}
I_{LY}	I_{LA}

★ TOPICS OF SELF-STUDY

★ Parallel operation of transformer
↳ The 4 condns to be satisfied.


★ SCOTT connection — 3 phase to 2 phase conversion.

Electrical Machines Notes

Chapter - 7

DC Machines

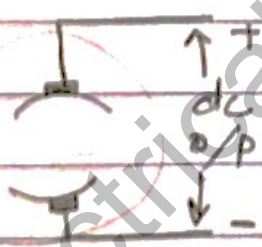
- * Even in DC machine, whatever is there inside a conductor, is alternating in nature.
- * Electric reaction = electric train.
- * DC machine symbol:-



voltage/current becomes unidirectional as the rings of commutator get exchanged b/w brushes while motion.

Commutator
 (B)
 ?

Brush Voltage

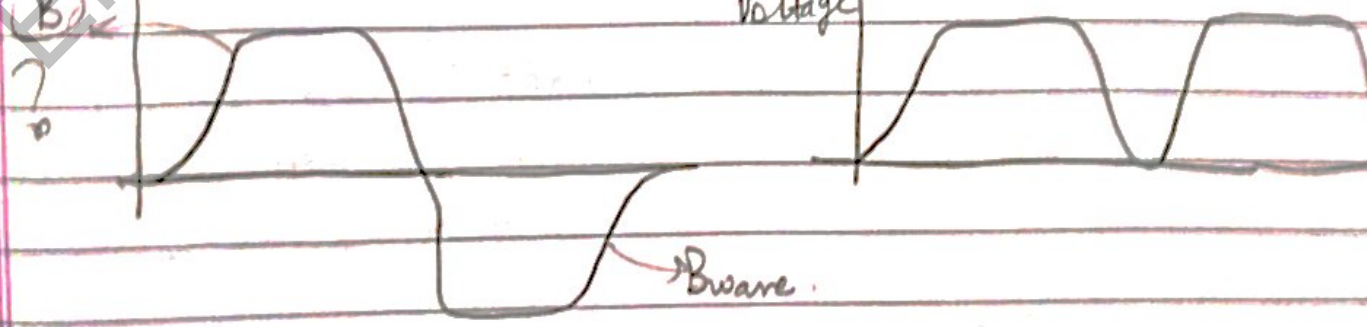

Chapter -10

★ EMEC: Electromechanical Energy Conversion

★ Armature windings

Lap winding

No. of ll paths $\frac{Z}{A}$
no. of poles (P)

(armature winding
is divided into n
ll paths)

Wave winding

No. of ll paths $\frac{Z}{A} = 2$ (always)

★ Conductor current (I_c) = $\frac{I_a}{A}$ → armature

★ Armature emf (E_a) = $\frac{\phi \omega_m Z}{2\pi} \left(\frac{P}{A}\right)$
= $k_a \phi \omega_m$

ϕ : flux per pole (Wb)

ω_m : armature speed (rad/s)

= $\frac{2\pi n}{60}$, where n is speed in rpm.

Z : total armature conductors

A : no. of ll paths

$k_a = \frac{ZP}{2\pi A}$

$$\text{or, } \boxed{E_a = \frac{\phi n Z (P)}{60} \text{ A}} : \text{EMF eq}^n$$

$$\begin{aligned} &\searrow \\ &E_a \propto \phi \omega_m \\ &\propto \phi n \end{aligned}$$

$$\text{Torque: } \boxed{\tau = \frac{1}{2\pi} \phi I_a Z \left(\frac{P}{P}\right) \text{ N-m}}$$

$$= \boxed{k_a \phi I_a} \text{ or}$$

$$\searrow \tau \propto \phi I_a$$

★ Power balance:-

$$\begin{aligned} \text{Mechanical power } \tau \omega_m &= k_a \phi \omega_m I_a \\ &= E_a I_a \\ &= \text{Electrical power.} \end{aligned}$$

★ Energy conservⁿ principle:-

Electrical & mechanical powers must balance in a machine.

$$\tau = \left(\frac{1}{\omega_m}\right) E_a I_a \text{ N-m,}$$

★ Linear Magnetisation

If magnetic circuit of machine is assumed linear, $\phi \propto I_f \Rightarrow \phi = k_f I_f$; I_f : field current

$$\begin{aligned} E_a &= k_a \phi \omega_m = k_a k_f I_f \omega_m = k_a k_f I_f \left(\frac{2\pi n}{60}\right) \\ &= k_e I_f n; \text{ where } k_e = k_a k_f \left(\frac{2\pi}{60}\right) \end{aligned}$$

specifically meant for motors.

Also, $T = k_a \phi I_a$
 $= k_a k_f I_f I_a = k_t I_f I_a$
 $\hookrightarrow k_t = k_a k_f$

Q. A 6 pole DC machine armature has 36 slots, 2 coil - sides / slot, 8 turns / coil & is lap wound. Flux/pole = 0.01 Wb

Find: Gross torque & mechanical power of
Given: when machine is operating as a motor at 1200 rpm with $I_a = 40 A$

$P = 6$ given

$\Rightarrow A = 6$ (lap wound)

$\Rightarrow \frac{P}{A} = 1$

No. of armature conductor, $Z = 36 \text{ slots} \times \frac{2 \text{ coil sides}}{\text{slot}} \times \frac{8 \text{ turns}}{\text{coil}}$
 $= 576$

E_a , induced emf = $\frac{\phi n Z (P)}{60 A}$

$= \frac{0.01 \times 1200 \times 576}{60 \times 1}$


$\Rightarrow E_a = 115.2 V$

$$\begin{aligned} \text{Gross Mechanical power} &= E_a I_a \\ &= 1152 \text{ W} \\ &= 1.15 \text{ kW} \end{aligned}$$

$$\text{Gross Torque (N-m)} = \frac{1152 \times 60}{2\pi \times 1200 \times 10^3}$$

$$\Rightarrow T = 9.1719 \text{ N-m}$$
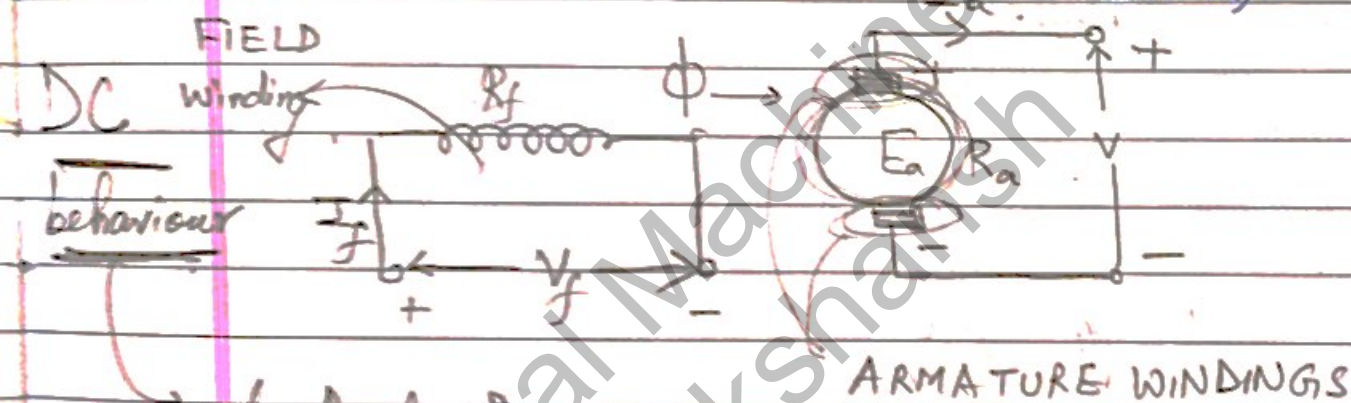
$$\star \text{ Gross Mechanical Power (W)} = \frac{\text{Gross Torque (N-m)} \times 2\pi n}{60}$$



only R_f & R_a

are shown. No role of X_L ($\because X_L = \omega L$
 $= 2\pi f L$)

$$\Rightarrow X_L = 0 \quad \text{for DC}$$

\star Generating mode:

The machine operates in generating mode (puts out electrical power) when I_a is in the dirⁿ of induced emf E_a as in fig. 7.6(a). For the armature circuit,

$$V (\text{terminal voltage}) = E_a - I_a R_a ; E_a > V$$

- The mechanical power converted to electrical form is :

$$P_{\text{mech}}(\text{in})|_{\text{net}} = E_a I_a = P_{\text{elec}}(\text{out})|_{\text{gross}}$$

- The net electrical power output is

$$P_o = \underbrace{V}_{\text{terminal voltage}} I_a$$

Also, $E_a I_a - V I_a = I_a^2 R_a = \text{Armature copper loss}$

$$\& P_{\text{mech}}(\text{in})|_{\text{gross}} = \text{shaft power} = P_{\text{mech}}(\text{in})|_{\text{net}} + \text{Rotational loss}$$

★ Motoring Mode:

$$V (\text{terminal voltage}) = E_a + I_a R_a ; V > E_a$$

- Electrical Power converted to mechanical form is

$$P_{\text{elec}}(\text{in})|_{\text{net}} = E_a I_a = P_{\text{mech}}(\text{out})|_{\text{gross}}$$

- Electrical power i/p is $P_i = V I_a$

Also, $V I_a - E_a I_a = I_a^2 R_a = \text{armature copper loss}$

$$\& P_{\text{mech}}(\text{out})|_{\text{net}} = \text{shaft power} = P_{\text{mech}}(\text{out})|_{\text{gross}}$$

- Rotational loss.

* electrical load \rightarrow eg: resistance.

In this mode, torque (τ) of electromagnetic origin is in the dirⁿ of armature rotⁿ i.e. mechanical power is put out and is absorbed by load (mechanical)
 \rightarrow eg: a generator, steam turbine

(P. 7.2) $E_a \propto n \phi$

or $n \propto \frac{E_a}{\phi}$

$$I_a = \frac{P}{V}$$

$$(E_a)_{gen} = V + I_a R_a$$

$$(E_a)_{motor} = V - I_a R_a$$

$$\phi_{motor} = \left(1 + \frac{10}{100}\right) \phi_{generator}$$

$$\frac{n_{gen}}{n_{motor}} = \frac{(E_a)_{gen}}{(E_a)_{motor}} \times \frac{\phi_{motor}}{\phi_{gen}} \quad \checkmark$$

* PM: Prime mover

Ex A DC shunt generator driven by a belt from an engine runs at 750 rpm while feeding 100 kW of electric power into 230 V mains. When the belt breaks, it continues to run as a motor drawing 9 kW from the mains. At what speed would it run? Given - Armature resistance is 0.08 Ω & field resistance is 115 Ω

Generator $\rightarrow 230$

$I_f = \frac{V}{R}$ $\rightarrow 115$ \therefore Remains const. in genⁿ change-over

$I_L = \frac{P}{V}$ $\rightarrow 10 \text{ kW}$ $\rightarrow 230$ has to be assumed in any problem.

$I_a = I_L + I_f$ (KCL)

$E_a (g) = V + I_a R_a$

$n_a (g) = 750 \text{ rpm}$ $\rightarrow 0.08$
 \rightarrow Given.

Motor

$I_L = \frac{P}{V}$ $\rightarrow 9 \text{ kW}$ $\rightarrow 230$

I_f (same as above = $\frac{V}{R}$)

$I_a = I_L - I_f$ (KCL)

$E_a (m) = V - I_a R_a$

Note :- Field current (I_f) didn't change during this operⁿ (of both kinds). So,
 E_a (emf induced) $\propto n_a$ (armature speed).
 Actually, $E_a \propto n \phi$ But ϕ is constⁿ ($\because I_f$ is constⁿ) So, in all, $E_a \propto n_a$

$$\begin{aligned} \text{So, } E_a(g) &= \frac{n_a(g)}{n_a(m)} \\ \Rightarrow n_a(m) &= \left[n_a(g) \right] \frac{E_a(m)}{E_a(g)} \\ &= 750 \times \frac{229.3}{237.8} \end{aligned}$$

$$n_a(m) = 723.1917 \text{ rpm}$$

* The axis in which brushes are located is called Quadrature axis (q-axis)
axis \perp to brushes, its called Direct axis (d-axis)

- * MNA: Magnetic Neutral Axis (Also called zero flux pt.)
- * Compensating winding (kept at ^{brush axis} wave pole) are put to prevent armature rxn.

Q. A separately excited DC generator has $R_a = 0.1 \Omega$, total brush drop = 2V. $N_1 = 1000 \text{ rpm}$ $I_{L1} = 100 \text{ A}$ at 250V. If $N_2 = 700 \text{ rpm}$, with I_f unchanged find current delivered to load.

$$R_L = \frac{V}{I}, \quad E_g = V + I_a R_a + \text{Brush drop}$$

$$E_{g1} \propto I_f N_1 \Rightarrow \frac{E_{g1}}{E_{g2}} = \frac{N_1}{N_2} \rightarrow E_{g2} \checkmark$$

$$E_{g2} = V + \underbrace{(I_{a2})}_{?} R_a + \text{Brush drop} \rightarrow I_{a2} ?$$

Q DC shunt motor

$$V = 220 \text{ V}$$

$$N_1 = 500 \text{ rpm}, R_a = 0.2 \Omega$$

$$I_{a1} = 50 \text{ A}$$

T is doubled.

Torque Find: new N_2

$$T \propto \phi I_a$$

$$\propto I_a \quad (\phi: \text{constt})$$

$$\Rightarrow \frac{T_1}{T_2} = \frac{I_{a1}}{I_{a2}}$$

$$2T_1 \Rightarrow \frac{1}{2} = \frac{I_{a1}}{I_{a2}} \Rightarrow I_{a2} = 2I_{a1} = 100 \text{ A}$$

Now, $E_a \propto N$

$$\Rightarrow \frac{E_{a1}}{E_{a2}} = \frac{N_1}{N_2} \rightarrow 500$$

$$\frac{V - I_{a1} R_a}{V - I_{a2} R_a} = \frac{N_1}{N_2} \rightarrow ?$$

$$V - I_{a1} R_a$$

$$V - I_{a2} R_a$$

$\rightarrow ?$

Q, A shunt generator delivers 50 kW, 250 V, 400 rpm
 $R_a = 0.02 \Omega$, $R_f = 50 \Omega$

What is speed of machine if it runs as a shunt motor, taking 50 kW i/p at 250 V.


$$\Rightarrow I_L \left(\frac{P}{V} \right)$$

Generator: $I_a = I_L + I_f$; $E_a = V + I_a R_a$

Motor: $I_a = I_L - I_f$; $E_a = V - I_a R_a$

$$E_a \propto I_f N$$

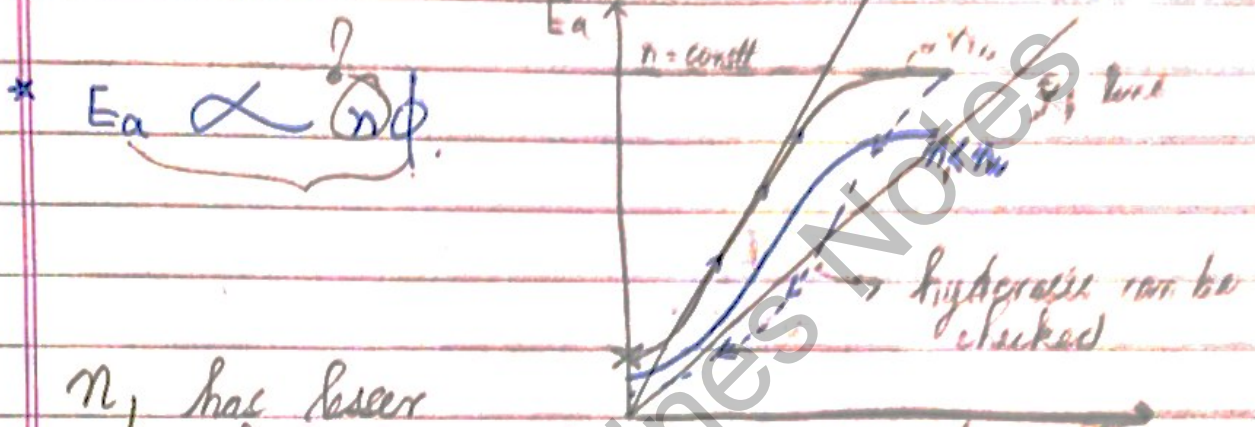★ NO-LOAD Saturation Characteristics } of DC
 or Open Circuit Characteristics (OCC) } generator
 or Magnetizing Characteristics }



n_1 has lesser value of n (comes before n_2) $\Rightarrow E \propto \phi n I_f$

We can reduce n_1 only till the airgap line doesn't coincide with R_f line. So, the min. value of n_1 that can come is : CRITICAL SPEED



★ Condns for build-up of voltage of generator:

1. Residual magnetism must be present in the poles.
2. For given direction of rotation, shunt field & coils should be so connected that E_a reinforces emf produced initially due to residual magnetism.
3. $R_f <$ Critical resistance.

Imp example
7.8

★ Characteristics of DC Generator


Separately excited

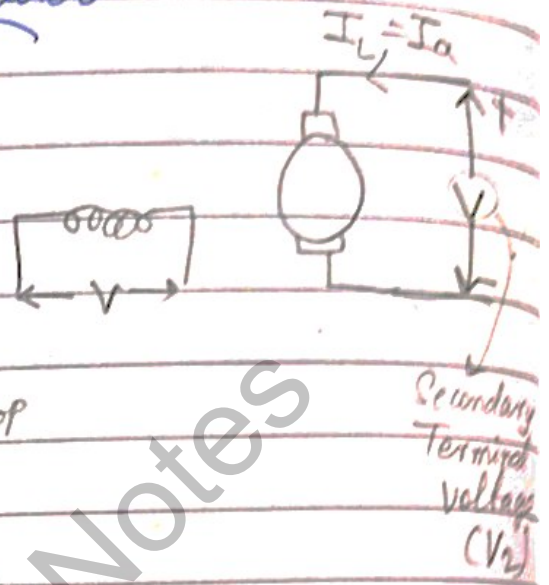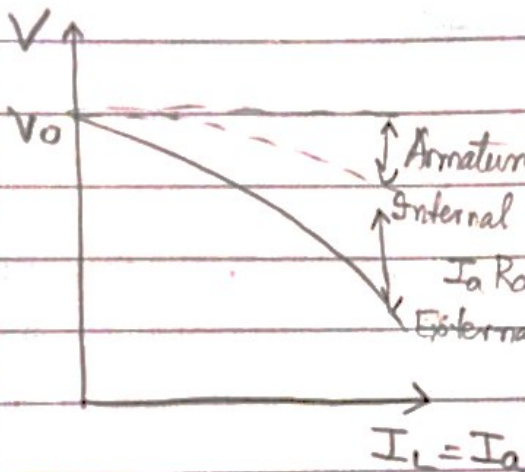


★ Rated speed - I_f adjusted to give rated voltage at no load (V_0).

$V = E_a - I_a R_a$ — with no load, demagnetising effect of the armature $\downarrow \Phi$ /pole due to which $E_a \downarrow$.

Shunt generator (Self excited generator)

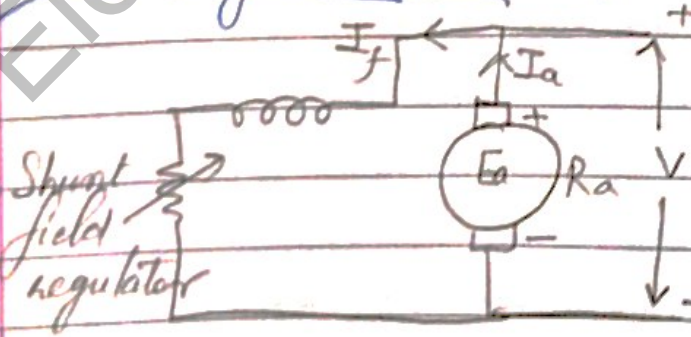

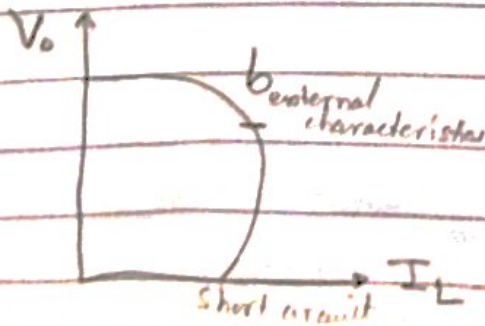Due to $I_a R_a$ drop & armature reaction, $V \downarrow$ more rapidly because $V \downarrow, I_f \downarrow$ & $\Phi \downarrow, E_a \downarrow$.




b: breakdown pt.

★ I_L : Load current : in generator
Line current : in motor

For currents \gg rated currents, beyond pt. b — due to severe armature rxn & \uparrow ed $I_a R_a$ drop drastic \downarrow in V than \uparrow in I_L .
As $I_c \uparrow$ further, generator is short circuit ($V=0$), though there is some E_a due to residual magnetism.


★ SERIES generator

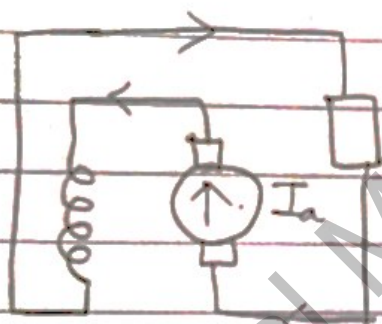

Field winding in series with armature & field carries I_a .
As load \uparrow , $I_a \uparrow$, $\phi \uparrow$, $E_a \uparrow$.

$$I_L = I_a = I_f$$

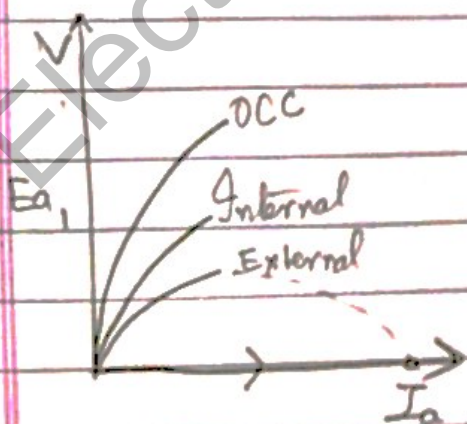Rising voltage charac.
At ~~no~~ high loads, armature rxn & $I_a R_a$ drop high, term. vol \downarrow




★ Characteristics of DC Motor

Motor: Imp. parameters: τ (torque), speed (n)
 Generator: " " : o/p power & Terminal voltage


$\tau = k_a \phi I_a$: Generator
 $\tau = k_T \phi I_a$: Motor

- $E_a = k_a \phi \omega$
- $n = k_N \frac{E_a}{\phi}$

Shunt motor

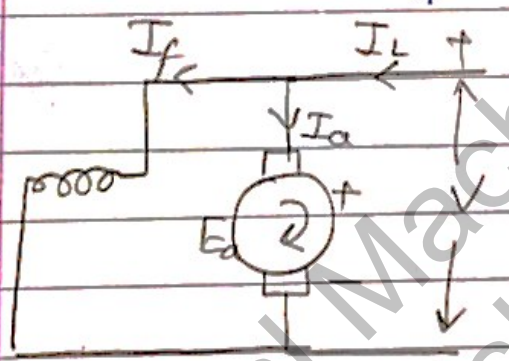

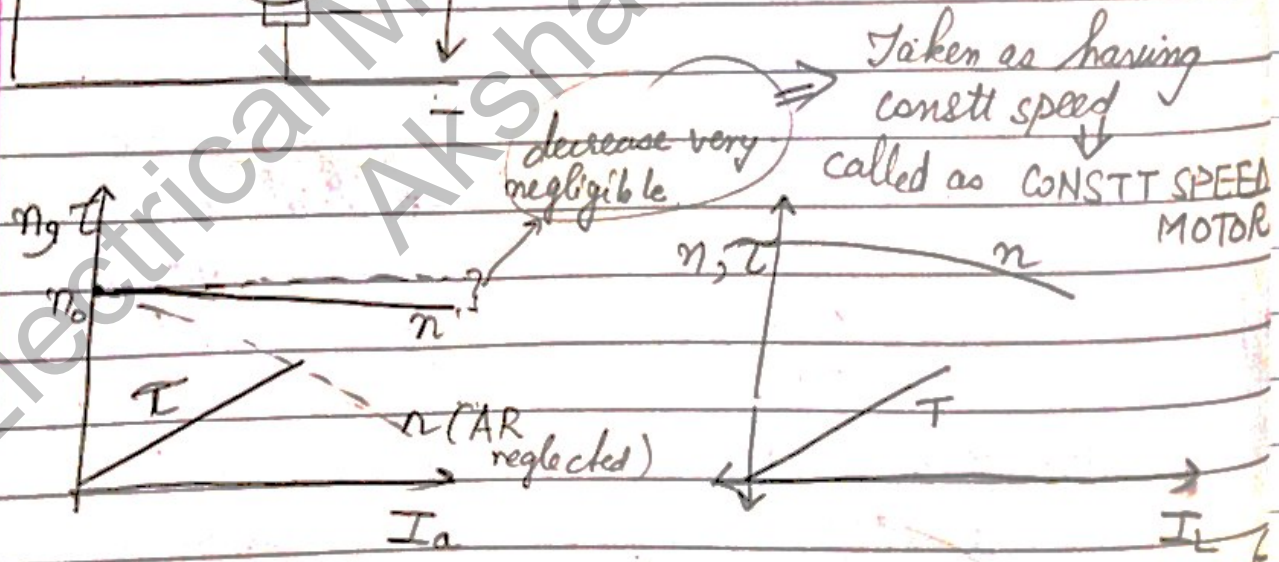$E_a = V - I_a R_a$
 $n = k_N \frac{(V - I_a R_a)}{\phi}$
 $\tau = k_T \phi I_a$



• Decrease in ϕ due to armature reaction in shunt motor
 ↳ compensates for \downarrow in n with E_a (graph)

$\tau - I_a$ graph: st. line without AR (Armature reaction)

• Constt. speed characteristics

$n = \frac{k_N}{\phi} - \left[\frac{k_N R_a}{k_T \phi^2} \right] \tau$; $\phi \propto I_f$

Series motor



$$n = k_N \left(\frac{V - I_a (R_a + R_{se})}{\phi} \right) \rightarrow \textcircled{1}$$

$$T = k_T \phi I_a$$

$$\phi = k_f I_f = k_f I_a$$

$$n = \frac{k_N}{k_f} \left[\frac{V}{I_a} - (R_a + R_{se}) \right]$$

(from ①)

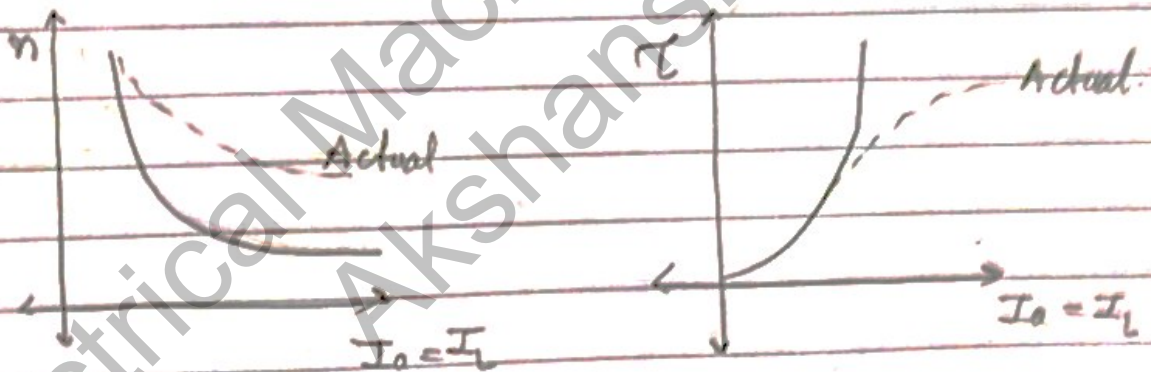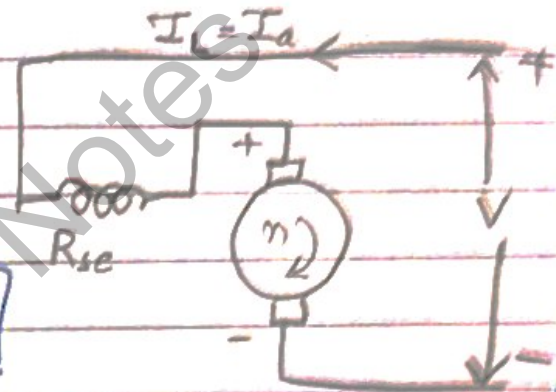

$n=0$ when $I_L=0$,

so, for no load, $n=0$

↓
don't turn series motor at no load ($I_L=0$)
∴ it can be damaged.

- Railway / Traction motor : applicⁿ of DC series motor

In this case

$$\phi \propto I_a$$

$$\& T \propto \phi I_a$$

$$\Rightarrow T \propto I_a^2$$

- suitable for trains etc.
- for starting a large accelerating torque,


- From $n-I_a$ eqⁿ, $I_a < 0$, $n \rightarrow \infty$.
 At no load, speed $\rightarrow \infty$.
 So, series motor should never be run on
 NO LOAD.

$$n = \frac{k_N}{k_f} \left[\frac{V}{I_a} - (R_a + R_{se}) \right]$$

$\hookrightarrow \tau = k_t k_f I_a^2$

$$\Rightarrow n = \frac{k_N}{k_f} \left[\frac{V \sqrt{k_t k_f}}{\sqrt{\tau}} - (R_a + R_{se}) \right]$$
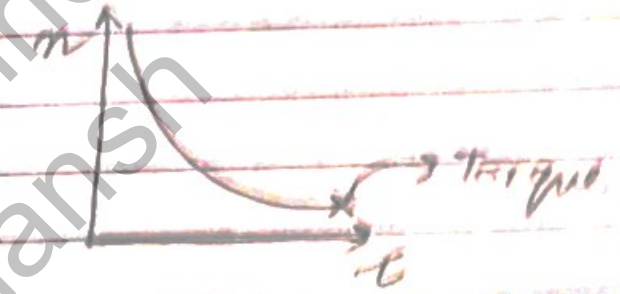
$$\Rightarrow n \propto \frac{1}{\sqrt{\tau}}$$



★ DC MACHINE 2 STD. FORMULAS

$\underbrace{\text{emf}}_{\text{eg}^n} = \left(\frac{\phi \omega Z}{60} \right) \left(\frac{P}{A} \right)$

flux speed no. of parallel conductors no. of poles
no. of paths

- Lap winding is $P = A$
- Wave winding is $A = 2$

$$E_a = V + I_a R_a = \text{Generator}$$

$$E_a = V - I_a R_a = \text{Motor}$$

$$\Rightarrow E_a = \phi \left(\frac{2\pi n}{60} \right) \left(\frac{zP}{2\pi A} \right)$$

ω angular speed in radians/s
 fixed for a machine.
 $= K_a$ (constt)

$$\Rightarrow \boxed{E_a = K_a \phi \omega}$$


2) Torque eqⁿ

In any electromechanical device
 Mechanical power = Electrical power.



$$\Rightarrow \boxed{T = K_a \phi I_a}$$

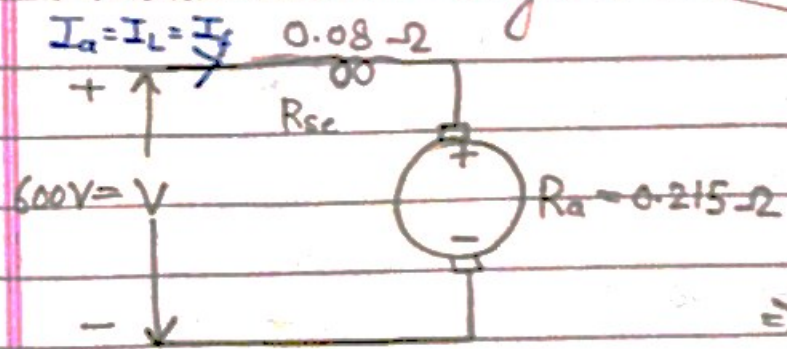Q A 60 kW, 600 V series railway motor has
 $R_a = 0.215 \Omega$, $R_f = 0.08 \Omega$. At rated voltage
 & at a current of 80 A, the speed is 750 rpm.
 Find the speed & torque when current = 95 A
 Assume linear magnetisation characteristics



$\Rightarrow \phi \propto I_f$
 $\Rightarrow \phi = K_f I_f$
 $E_a = K_a (K_f I_f) I_a$
 $\Rightarrow E_a = K_a K_f I_a I_a$

At rated voltage, $I_a = 80 \text{ A}$

$$\star E_{a1} = V - I_{a1} (R_a + R_{se})$$

↳ this additional factor comes in case of D.C. series motor

$$= 600 - 80(0.08 + 0.215)$$

$$= 600 - 8(2.95)$$

$$\Rightarrow E_{a1} = 576.4 \text{ V}$$

Now,

$$E_a = K_a \phi \omega$$

$$= K_a (K_f I_f) \omega$$

$$\Rightarrow E_{a1} = (K_a K_f) I_{a1} \left(\frac{2\pi n_1}{60} \right) \rightarrow \textcircled{1}$$

$$\Rightarrow (K_a K_f) = \frac{(576.4) \times 60}{80 \times 2\pi (750)} = 0.09178$$

K_a', say

Now, $I_{a2} = 95 \text{ A}$

$$E_{a2} = V - I_{a2} (R_a + R_{se})$$

$$= 600 - 95(0.08 + 0.215)$$

$$= 600 - 9.5(2.95)$$

$$\Rightarrow E_{a2} = 571.975$$

$$\Rightarrow E_{a2} = (K_a K_f) I_{a2} \left(\frac{2\pi n_2}{60} \right) \rightarrow \textcircled{2}$$

$$\Rightarrow \frac{E_{a1}}{E_{a2}} = \frac{I_{a1}}{I_{a2}} \left(\frac{n_1}{n_2} \right) \rightarrow \textcircled{1} \div \textcircled{2}$$

$$\Rightarrow n_2 = \left(\frac{I_{a1}}{I_{a2}} \right) \left(\frac{E_{a2}}{E_{a1}} \right) (n_1)$$

$$= \left(\frac{80}{95} \right) \left(\frac{571.975}{576.4} \right) (750)$$

$$\Rightarrow n_2 = 626.73 \text{ rpm.}$$

Also

$$T = K_a \phi I_a$$

$$\Rightarrow T = K_a (K_f I_f) I_a$$

$$= K_a K_f I_a I_a$$

$$= (K_a K_f) I_a^2$$

$$= 828.345 \text{ Nm.}$$

0.09178 ($T \propto I_a^2$)

Aliter

$$\omega T = E_a I_a$$

$$\frac{2\pi n}{60}$$

Q. A 20 V DC series motor has linear OCC, with a slope of 12 V / field ampere at 1200 rpm. Find the speed at which the motor will run when developing T of 40 Nm. What current would it draw from the mains?

Given: $R_a + R_{se} = 0.6 \Omega$

$$E_{a1} = V - I_{a1} (R_a + R_{se})$$

$$E_a = (K_a K_f) I_a^2 \omega$$

12 V per field ampere

$$\Rightarrow 12 = K_a' (1) \left(2\pi n \frac{1200}{60} \right) \Rightarrow K_a' = 0.0955$$

$$T = K_a \phi I_a$$

$$= K_a K_f I_a I_a$$

$$\Rightarrow I_a^2 = \frac{T}{K_a}$$

$$\Rightarrow I_a = \sqrt{\frac{40}{0.0955}}$$

$$\Rightarrow I_a = 20.465$$

$$\omega = ?$$

$$\hookrightarrow \text{Idea} \therefore E_{a1} = V - I_a (R_a + R_{se})$$

$$E_{a1} = K_a' I_a (\omega)$$

$$E_{a1} = 250 - 20.465 (0.6)$$

$$\Rightarrow E_{a1} = 237.721$$

$$\Rightarrow \omega = \frac{237.721}{(0.0955) (20.465)}$$

$$\omega = 121.633 \text{ rad/s}$$

$$\omega = \frac{2\pi n}{60}$$

$$\Rightarrow n = \frac{\omega \times 60}{2\pi}$$

$$\Rightarrow n = 1162.101 \text{ rpm}$$

Ans

Q A DC shunt motor runs at 1200 rpm on no load drawing 5A current from 220 V mains.

When loaded, the motor draws 62A ($I_L = 62$ A)

What would be speed? ($n = ?$)

Assume: armature rxn demagnetises the field by 5%.

$$\text{i.e. } \phi_1 = (0.95) \phi_0$$

Also calculate internal torque developed at no load & load cond^{ns}. What is the shaft torque available at load cond^{ns} specified ($T_{\text{shaft}} = T_1 - T_0$)

Given :- $R_a = 0.25 \Omega$

$$R_{sh} = R_f = 110 \Omega$$

$$I_{a0} = I_{L0} - I_f = 5 - \frac{220}{110} = 3 \text{ A}$$

no
load

$$E_{a0} = V - I_{a0} R_a = 220 - 3(0.25) = 219.25$$

$$= k_a \phi_0 \omega_0$$

$$= k_a \left(\frac{2\pi}{60} \right) \phi_0 n_0 = k_a k_f \left(\frac{2\pi}{60} \right) I_f (n_0)$$

$$T_0 = k_a \phi_0 I_{a0} = k_a \phi_0 (3)$$

$$= k_a k_f I_f (3)$$

$$E_{a0} = 219.25 = k_a k_f \left(\frac{2\pi}{60} \right) (3) \left(\frac{1200}{60} \right)$$

$$\Rightarrow k_a k_f = \frac{(219.25)}{80\pi} = 0.8728$$

$$T_0 = \left(\frac{219.25}{80\pi} \right) \times 3$$

$$= 5.23 \text{ Nm}$$

load $I_{L1} = 62 \text{ A}$

$$\phi_1 = (0.95) \phi_0$$

$$I_{a1} = I_{L1} - I_f = 62 - 2 = 60 \text{ A}$$

$$E_{a1} = V - I_{a1} R_a = 220 - (60)(0.25)$$

$$E_{a1} = 205 \text{ V}$$

$$= k_a \phi_1 \left(\frac{2\pi n_1}{60} \right)$$

$$= k_a (0.95) \phi_0 \left(\frac{2\pi n_1}{60} \right)$$

Now

$$E_{a1} = (k_a \phi_0) \left(0.95 \times \frac{2\pi n_1}{60} \right) = 205$$

$$\Rightarrow k_a \phi_0 = \frac{205 \times 60}{2\pi n_1 \times 0.95} \rightarrow \textcircled{1}$$

$$\& E_{a0} = (k_a \phi_0) \left(\frac{2\pi n_0}{60} \right) = 219.25$$

$$\Rightarrow k_a \phi_0 = \frac{219.25 \times 60}{2\pi n_0} \rightarrow \textcircled{2}$$

$\textcircled{1}$ & $\textcircled{2}$

$$\Rightarrow \frac{205 \times 60}{2\pi n_1 \times 0.95} = \frac{219.25 \times 60}{2\pi n_0}$$

$$\Rightarrow n_1 = \frac{205 \times n_0}{219.25 \times 0.95} = \frac{205 \times 1200}{219.25 \times 0.95}$$

$$\Rightarrow n_1 = 1181.059$$

$$\Rightarrow n_1 = 1181.059$$

$$T_1 = k_a \phi_1 I_{a1}$$

$$= k_a \phi_0 (0.95) I_{a1}$$

$$= \left(\frac{219.25 \times 60}{2\pi \times 1200} \right) (0.95) (60)$$

$$\Rightarrow T_1 = 995.003 \text{ Nm}$$

$$T_{sh} = T_1 - T_0$$


$$\Rightarrow T_{sh} = 989.77 \text{ Nm}$$

★ EFFICIENCY OF DC MACHINE

★ Power flow diagram for


GENERATING Mode :

$$(P_{mech})_{in} = E_a I_a$$

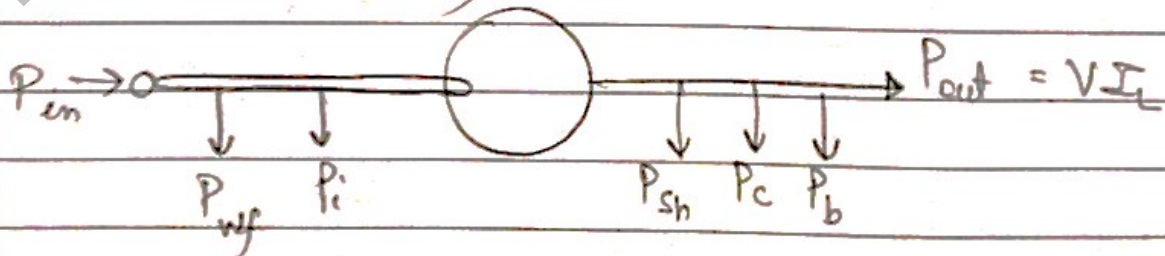

MOTORING Mode
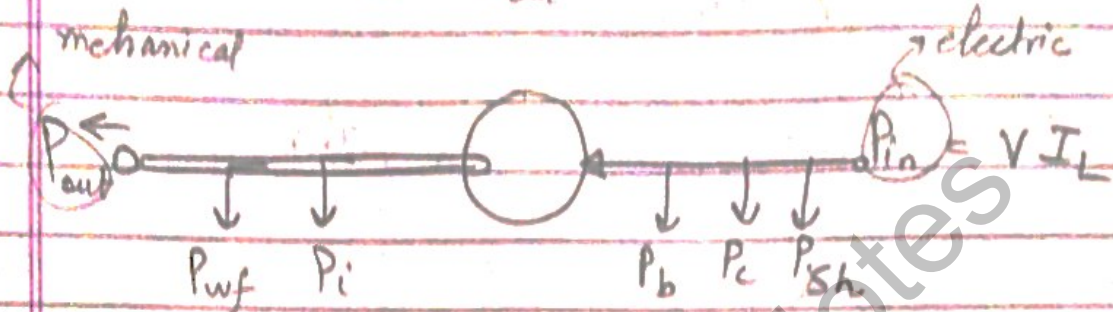
$$(P_{\text{mech}})_{\text{out}} = E_a I_a$$



P_{wf} : friction & windage loss (or mechanical loss)

P_i : total core loss (no load iron loss, stray load iron loss)

P_{sh} : shunt field loss (in shunt machine)
(or field copper loss)

P_c : armature copper loss (including loss in series winding)

P_b : brush contact loss.

Alternative terms :

$P_{wf} + \text{no load iron loss} = \text{total losses } (P_{\text{tot}})$

P_{wf} : mechanical losses.

Q. A 600 V DC shunt motor drives a 60 kW load at 900 rpm.

$$R_f = R_{sh} = 100 \Omega$$

$$R_a = 0.16 \Omega$$

$$P_{\text{out}} = 60 \text{ kW}$$

$$\text{Motor } \eta = 0.85 = 85\%$$

Find (a) Retnal loss (P_{ret})

(b) no load armature current (I_{a0})

(c) Speed. (m)

(d) Speed regulation

(e) armature current for electromagnetic torque of 600 Nm.


$$\eta = \frac{P_{out}}{P_{in}} \Rightarrow P_{in} = \frac{60 \times 10^3}{0.85}$$

$$\Rightarrow P_{in} = 70.5 \text{ kW}$$

$$\text{Now, } P_{in} = V \times I_L$$

$$\Rightarrow 70.5 \times 10^3 = 600 \times I_L$$

$$\Rightarrow I_L = 117.65 \text{ A}$$

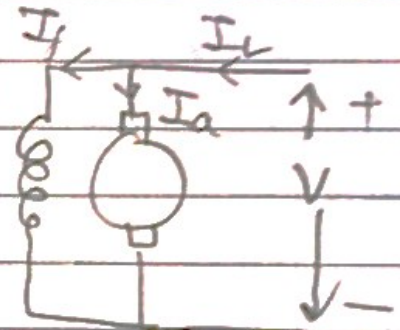

$$I_f = \frac{V}{R_f} = \frac{600}{100} = 6 \text{ A}$$

$$I_a = I_L - I_f$$

$$\Rightarrow I_a = 111.65 \text{ A}$$

$$\text{Now, } E_a = V - I_a R_a$$

$$= 600 - (111.65)(0.16)$$

$$\Rightarrow E_a = 582.14 \text{ V}$$

Now,

$$E_a = k_a \phi \omega = k_a \times \phi \left(2\pi \times \frac{900}{60} \right)$$

$$\Rightarrow k_a \phi = \frac{582.14 \times 60}{2\pi \times 900} = 6.1798$$

$$\begin{aligned}
 P_L &= \text{Total losses} \\
 &= \text{armature Cu loss} + P_{sh} + P_{rot} \\
 &= I_a^2 R_a + V I_f + P_{rot} \\
 &= (111.65)^2 \times 0.16 + (600)(6) + P_{rot}
 \end{aligned}$$

$$P_L = 5594.5156 + P_{rot}$$

Now

$$P_{in} = P_{out} + P_L$$

$$\begin{aligned}
 \Rightarrow P_L &= P_{in} - P_{out} \\
 &= 70.5 - 60 \text{ kW}
 \end{aligned}$$

$$\Rightarrow P_L = 10.5 \text{ kW}$$

$$\Rightarrow P_{rot} = P_L - 5.594 \text{ kW}$$

$$\Rightarrow P_{rot} = 4.906 \text{ kW}$$

(b) No Load Condition

$$V I_{a0} = P_{rot} + (I_{a0})^2 R_a$$

$$\Rightarrow 600 \times I_{a0} = 4906 + (I_{a0})^2 (0.16)$$

$$\Rightarrow (I_{a0})^2 - \frac{60,000}{16} I_{a0} + \frac{490600}{16} = 0$$

$$\Rightarrow (I_{a0})^2 - 3750 I_{a0} + 30662.5 = 0$$

In No load condⁿ, o/p is negligible.

So, whatever ip comes to motor, it totally gets used in losses.

$$\text{So, } V I_{ao} = P_{rot} + 0$$

$$\Rightarrow I_{ao} = \frac{P_{rot}}{V}$$

$$= \frac{4908}{600}$$

$$I_{ao} = 8.176 \text{ A}$$

ignoring the drop.

(c) Now, $E_{ao} = V - I_{ao} R_a \approx V$ (at no load)

$$= 600 - (8.176)(0.18)$$

$$= 600 \text{ V}$$

neglect

Now:

$$E_{ao} = (R_a \phi) \left(\frac{2\pi n_o}{60} \right)$$

$$\Rightarrow 600 = (6.1798) \left(\frac{2\pi}{60} \right) \times n_o$$

$$\Rightarrow n_o = \frac{600 \times 60}{2\pi \times 6.1798}$$

$$\Rightarrow n_o = 927.616 \text{ rpm}$$

(d) Speed regulation = $\frac{\text{no load speed} - \text{load speed}}{\text{load speed}} \times 100$

$$= \frac{927.616 - 900}{900} \times 100$$

$$= 3.068 \%$$

(e) Torque \rightarrow not I_{a0}

$$T = (k_a \phi) I_a$$

$$\Rightarrow 600 = 6.178 (I_a)$$

$$\Rightarrow I_a = 97.118 \text{ A}$$

thus

★ TESTING OF DC MACHINES


- Swinburne's test
 - Hopkinson's test
- non loading tests
- measuring losses & finding efficiency
- mostly conducted on shunt motor : for no loads in series current is very high & speed $\rightarrow \infty$.

★ HOPKINSON'S Test

Regenerative test in which two IDENTICAL DC shunt machines are mechanically coupled.

- One as DC generator, other as motor.
- The set of teeth draws power (only that much) that it can make up for losses from mains.
- (akin to Sumpner's test of transformer).

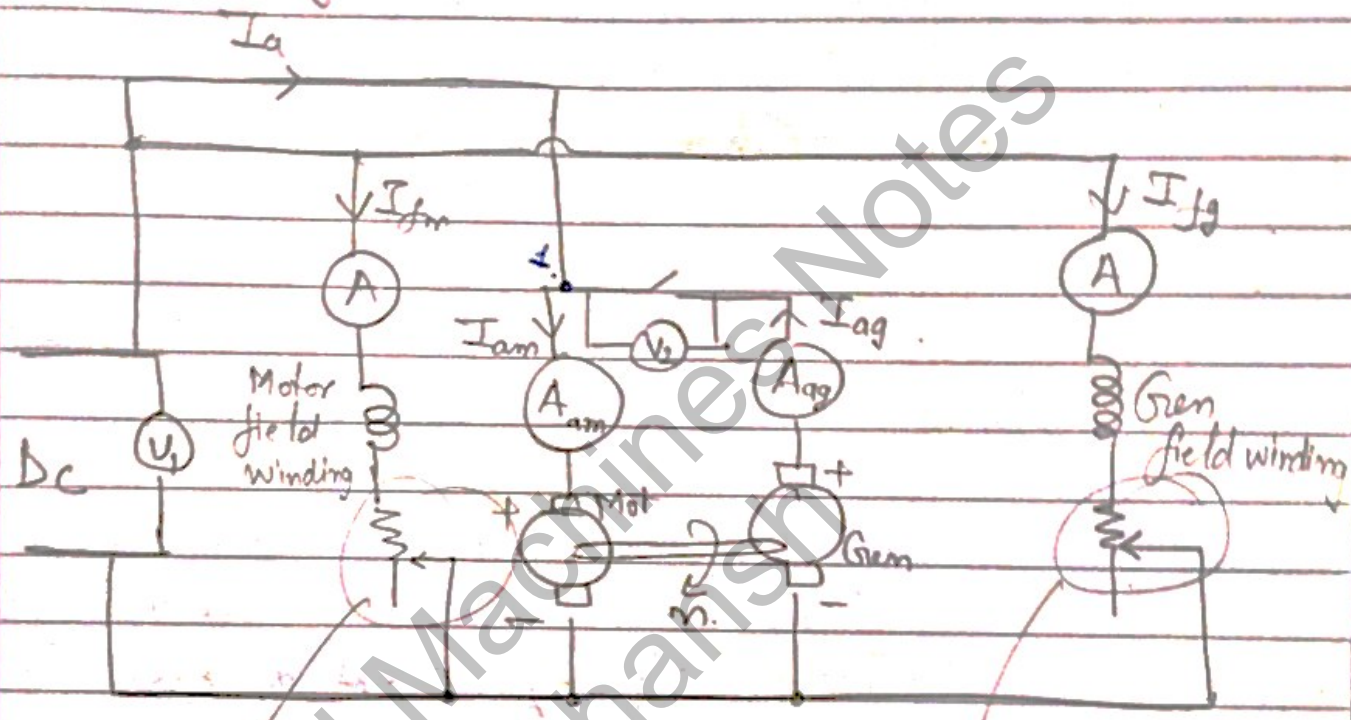* Why not direct loading tests?
 - eg. Suppose 6000 DC machines \rightarrow test each one with load \rightarrow lot of ϵ loss.
 - load might not be available.



✓ experiments
 vary field rheostat of motor is used to set motor to rated speed.

field rheostat of generator is used to set generator to rated voltage.

- S1) Motor made to run at rated speed.
- S2) Switch is closed after checking V_2 (reads zero or negligible) & similar polarities of machine are connected across switch S.

$$\begin{aligned}
 I_a &= \text{current drawn from supply} \\
 &= I_{am} - I_{ag}
 \end{aligned}$$

KCL at node 1,

$$I_a + I_{ag} = I_{fm} = I_{am}$$

$$\begin{aligned} \text{Total ip to armature circuit} &= V I_a \\ &= \text{Total armature loss} \\ &(\because \text{set of } p \rightarrow 0) \end{aligned}$$

$$V I_a = \text{armature Cu loss (generator)} + \text{armature Cu loss (motor)} + \text{Total stray loss}$$

$$I_{ag}^2 R_{ag}$$

$$I_{am}^2 R_{am}$$

$$\begin{aligned} \Rightarrow \text{Total stray loss} &= V I_a - I_{am}^2 R_{am} - I_{ag}^2 R_{ag} \\ &= (P_{wg} + P_{io}) + \text{Stray load loss} \\ &= (P_{rot} + \text{Stray load loss}) \end{aligned}$$

$$P_{\text{stray}} \text{ (each machine)} = \frac{1}{2} [V I_a - I_{am}^2 R_{am} - I_{ag}^2 R_{ag}]$$

assumed

- Q. Following results were obtained while Hopkinson's test was performed on 2 similar DC shunt machines:-
- Supply voltage = 250 V
- Field current of motor = 2 A = I_{fm}
- Field current of generator = 2.5 A = I_{fg}
- $I_{ag} = 60$ A
- $I_a = 15$ A (Current taken from supply)

$$R_{am} = R_{ag} = 0.2 \Omega$$

Calculate η of motor & generator under these cond^{ns} of load.

Motor

$$\begin{aligned} I_a + I_{ag} &= I_{am} \\ \Rightarrow 15 + 60 &= I_{am} \end{aligned}$$

$$P_{\text{stray}} = \frac{1}{2} \left[\sqrt{I_a^2 R_{am} + I_{ag}^2 R_{ag}} \right]$$

motor
I/P.

$$P_{\text{in, motor}} = V I_{am} + V I_{fm} \quad \checkmark$$

$$\text{Loss of motor} = P_{Lm} = \left(P_{\text{stray}} + V I_{fm} \right) + I_{am}^2 R_{am}$$

→ Field Cu loss

$$\eta_{\text{motor}} = \frac{P_{\text{in, motor}} - P_{Lm}}{P_{\text{in, m}}} = 86.6\%$$

→ Arm. Cu loss.

Generator

$$P_{Lg} = P_{\text{stray}} + V I_{fg} + I_{ag}^2 R_{ag}$$

$$P_{\text{out, g}} = V I_{ag}$$


$$\eta_g = \frac{P_{\text{out, g}}}{P_{\text{out, g}} + P_{Lg}} = 86.7\%$$

★ Self Study

- Q. What are the advantages of Hopkinson's test over Swinburne's test? What are its limitations?
- Q. Which type of losses cannot be determined by Swinburne's test and how are these estimated for calculating η ?

§ Starting of DC MOTOR

- 3-pt. starter

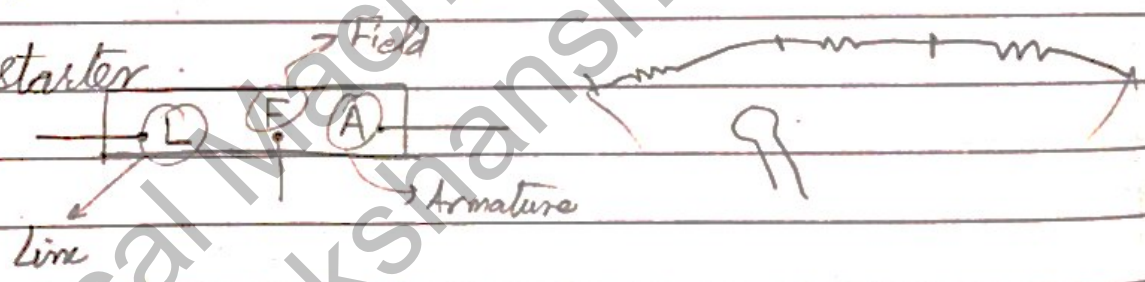

- DC motors are inherently self starting (∴ it'll start even if 3 pt. starter isn't there)

At start,

$$E_a = 0 \text{ (back emf } \approx 0 \text{)}$$

$$V - I_a R_a = 0$$

$$I_{a(\text{Start})} = \frac{V}{R_a} = \frac{220}{0.5} = 440 \text{ A}$$

→ very high

= INRUSH CURRENT ^{rated}
 ≈ 6-8 times ~~to~~ normal current
 So, 3-pt. starter used.

* $T_{\text{starting}} \propto$ resistance of armature circuit

↳ Higher the starting torque, it'll be able to lift heavy loads at start.

* If Inrush current left unhandled

- (i) heavy spark at brushes destroying commutators
- (ii) $I_{a(\text{start})}$ gives rise to high starting torque causing mechanical shock, \downarrow machine life
- (iii) supply fluctuation due to 'inrush' current.

• Max allowable starting current \times 1.5 to 2^{times} rated value

• Starter: at start, resistance fully included, gradually cut out as motor picks up speed to give a good torque.

* Protections in a Starter:

1. NVC (No Volt coil): Failure of I_f (due to accidental or \emptyset open circuit of field), this control releases handle (held electromagnetically) & goes back to OFF.
2. OL (over load) release: relay at $e > I_a$ (overload or short circuit) brings handle to OFF.

★ Self Study

Speed Control

- For shunt motor
 - (i) Field control (constt power control)
 - (ii) Armature control (constt. torque control)

$$n \propto \frac{E_b}{\phi}$$

$$\propto \frac{V - I_a R_a}{I_f}$$

→ Armature control
 → field control

Field control

Speed $\approx 1500 - 1800$ rpm

$$n > n_{rated}$$



V is constt (constt power)
"field weakening"



Armature control

$$n < n_{rated}$$

I_f is constt (constt torque)

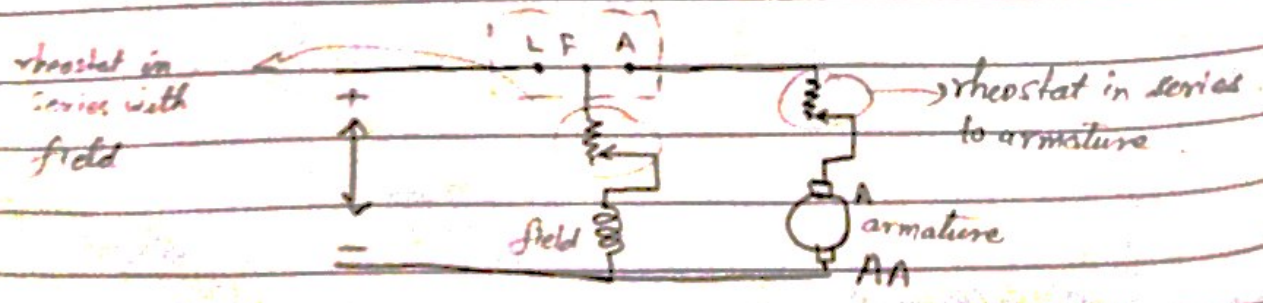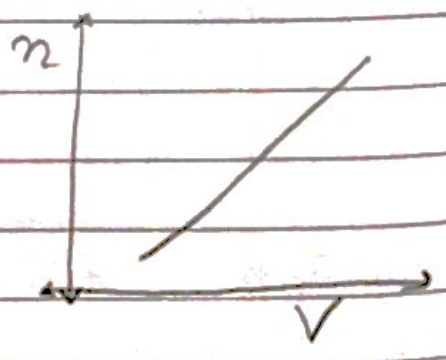

★ Self Test (4th Edition)

- * } Ex 7.6, 7.7, 7.8, 7.9, 7.32, 7.33, 7.34, 7.45, 7.58,
7.59, 7.62.
* } Q. 7.10, 7.12, 7.14, 7.17, 7.19, 7.26, 7.28, 7.30, 7.32,
7.35, 7.36, 7.40, 7.46, 7.47, 7.48, 7.50.

—*—

Electrical Machines Notes
Akshansh


★ Ch- 3 ϕ Induction motor.

★ For creating rotating magnetic field, consider 2 ϕ rotating magnetic field.

windings $\rightarrow 90^\circ$ displacement in space.

their currents $\rightarrow 90^\circ$ displacement in phase.

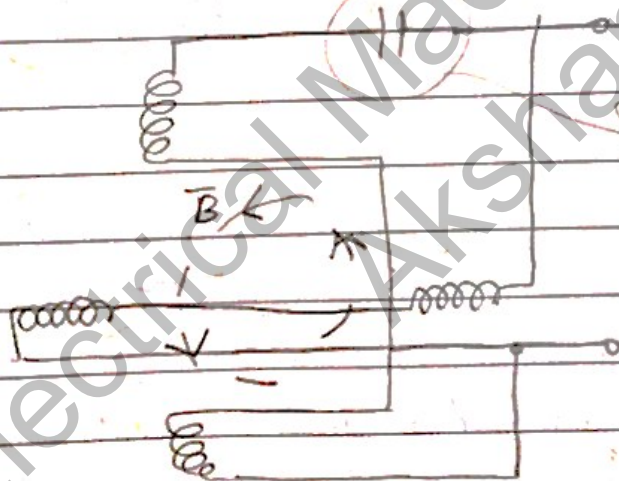Phase difference of 90° caused using a capacitor.



should have very large value for it to work


Solⁿ

Use 3ϕ induction motor

★ The field of the stator rotates at synchronous speed (n_s) ($f = \frac{n_s p}{120}$), where f is supply

frequency, p : no. of poles.

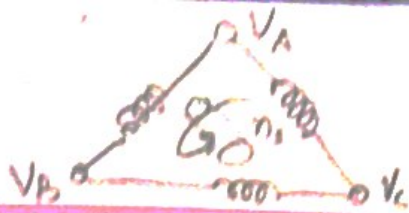★ The stator winding is wound for 3 ϕ displaced in space by 120° & whose currents have a phase shift of 120° , creates a rotating magnetic




field which revolves at n_s

The most popular type of rotor of a 3 ϕ induction motor is squirrel cage rotor which has rotor legs made of Cu/Al rather than winding

Singly phase motor: Supply is given only to stator

Squirrel cage rotor

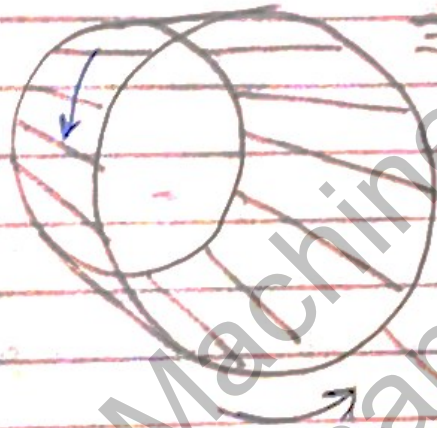

90% of motors of that type

- ∩ : conductors (not wires) - heavy bars of Cu, Al or alloys - kept in slots with short-circuiting end rings
- has lower starting torque

* WRIM: Wound Rotor Indⁿ motor: other type of Indⁿ motor (not that popular)

- also called: Slip ring Indⁿ motor
- has as many poles as stator poles
- has 3 leads brought out of machine via slip rings that are trapped by Cu-carbon brushes. Ext. resistance can be added in the rotor circuit. Hence, ↓ starting current → ↑ starting torque.

* Advantage of WRIM over squirrel cage

Add ext. resistance to motor:	WRIM	✓
	Squirrel cage	X

* Rotating magnetic field

If motor speed = motor field speed = n_s → synchronous speed.
 ↳ then, no relative speed \Rightarrow no emf \Rightarrow no current
 no torque to sustain rotation \Leftarrow
 So, rotor \downarrow runs at speed, $n < n_s$

• Slip, $s = \frac{n_s - n}{n_s} \times 100$ (in %)

• ; $n_s - n$: slip speed.

- Slip \uparrow with load, $\therefore n \downarrow$. Full load slip $\approx 3-10\%$.
- Here, singly fed machine is stator fed unlike sync. m/c
- These machines don't run at n_s $\therefore T$ is ^{not} possible at n_s .
 So, they are called asynchronous machines.

* Circuit model

§ Generalised transformer in which rotor emf & frequency both depend on rotor speed.
 ↳ conversion of energy takes place

↳ V_1 : applied voltage / phase

↳ K_{w1} : stator winding factor

↳ N_{ph1} : stator series turns / phase

• $\frac{E_1}{E_2} = \frac{K_{w1} N_{ph1}}{K_{w2} N_{ph2}} = a$ (turns ratio)

• Rotor frequency at any speed n , $f_2 = sf$ → slip
→ stator frequency

• I_0 (exciting current) : 40% of FL current.
 or no load current

In a transformer,


%age of FL current taken by no load current

Q. Why I_m shouldn't be operated at no/light loads for long periods of time?

• Rotor impedance, $Z_2 = R_2 + j s X_2$

Rotor resistance

standstill rotor leakage reactance.

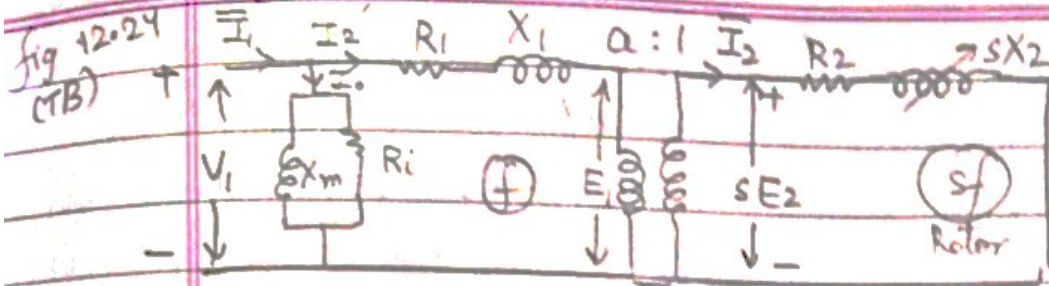

Stator P_G \rightarrow P_m (mech)


Supply frequency = f \rightarrow Rotor side $\omega = sf$ \rightarrow slip

$$\bar{I}_2 = \frac{sE_1}{R_2' + jX_2'} = \frac{E_1'}{R_2' + jX_2'}$$

$$P_m = \frac{(I_2')^2 R_2'}{s} - (I_2')^2 R_2' = (I_2')^2 \left(\frac{1}{s} - 1 \right) R_2'$$

$$R_L = R_2' \left(\frac{1}{s} - 1 \right)$$

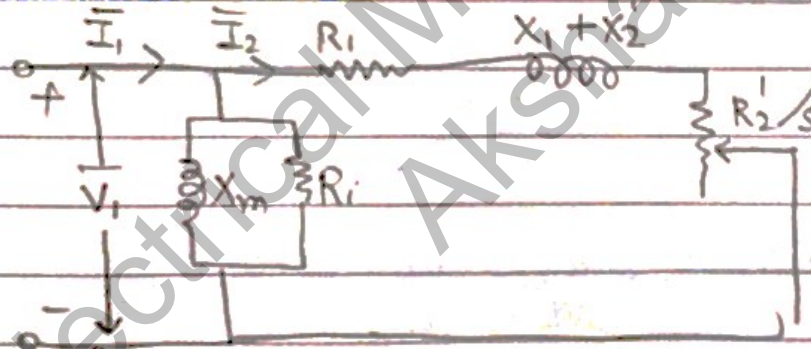* Generalised t/f in which frequency is also transformed in proportion of slip (s) st rotor emf = sE_2 & rotor reactance = sX_2



: Approx. model.
: Shunt branch shifted to front.

• Power across air gap

$$P_G = \frac{(3I_2')^2 R_2'}{s} = \frac{3I_2'^2 R_2'}{s}$$

= rotor Cu loss / slip

$$\Rightarrow \text{Rotor Cu loss} = \text{slip} \times P_G$$

* Gross mech. power o/p = $P_m = P_G - \text{electrical loss in rotor resistance}$

$$= P_G - 3(I_2')^2 R_2' = 3(I_2')^2 R_2' \left(\frac{1}{s} - 1 \right)$$

$$\Rightarrow P_m = (1-s) P_G \quad \star$$

Electromagnetic torque (T) = $\frac{P_m}{\omega}$ rotor speed in rad/s

or
(shaft torque) $= \frac{3(I_2')^2 R_2 (1/s - 1)}{(1-s) \omega_s} = (1-s) \omega_s$

or
(useful torque) $= \frac{3(I_2')^2 R_2 / s}{\omega_s} = \frac{P_G}{\omega_s} \text{ N-m}$


$\Rightarrow P_G = T \omega_s$
 = Torque in Sync. watts

- note
- When IM runs, it runs less than rated speed.
 - slip is always +ve for IM.
 - Subsynchronous speed I.G runs at $n > n_s$: slip -ve
 - Super synchronous speed slip will never be 0.


So, Net mech. power o/p = $P_m - (\text{windage, friction, stray load losses})$

Summary :- $P_m = \omega T$: shaft power o/p
 $P_G = \omega_s T$

Power stages in IM

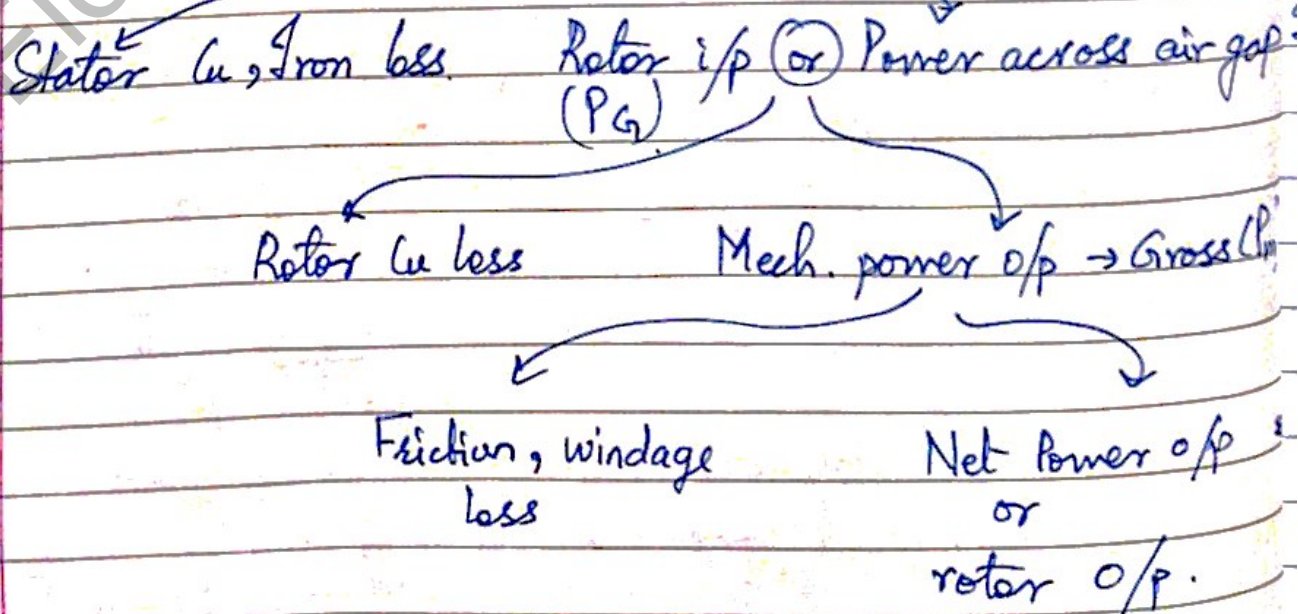

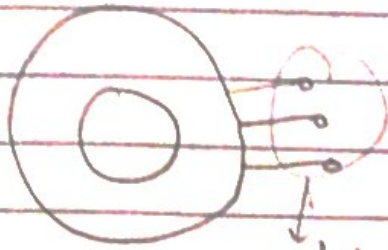* Torque-Speed characteristics of Induction motor.



3 ϕ induction motor

n_s : synchronous speed
: Stator FIELD rotates at this speed

* Rotor rotates at speed $< n_s$ (n)

* $n_s = \frac{120f}{P}$ \rightarrow stator frequency
 P \rightarrow no. of poles.

* Slip, s (%) = $\frac{n_s - n}{n_s} \times 100$

\rightarrow At start, $n = 0$. So,
 $s = 1$ or 100%

\rightarrow s is always +ve for indⁿ motor ($\because n < n_s$)

* Induction generator

Slip, s is -ve ($\because n > n_s$)

Indⁿ generator (n) Speed higher than n_s : Super synchronous speed
Indⁿ motor : n lower than n_s : Sub synchronous speed.

* Rotor can never run at n_s .
So, slip $\neq 0$. (never = 0)

Q Find n_s ; rotor speed, n ; & I_2 of rotor current of a 3ϕ ind^m motor with stator poles $(P) = 4$ & a slip of $(s) 0.03\%$.

f : stator frequency = 50 Hz (assume)

$$(a) n_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

(b) frequency of rotor current = slip \times supply frequency
 $\Rightarrow f_2 = s \times f$

Now

$$0.03 = \frac{1500 - n}{1500} \Rightarrow 45 = 1500 - n$$


$$\Rightarrow n = 1455 \text{ rpm}$$

$$\Rightarrow I_2 = 0.03 \times 50 = 1.5 \text{ Hz}$$

* Note:- NO SLIP \equiv NO INDUCTION MOTOR.

* Torque Speed Characteristics

also called
PULL
OUT
torque

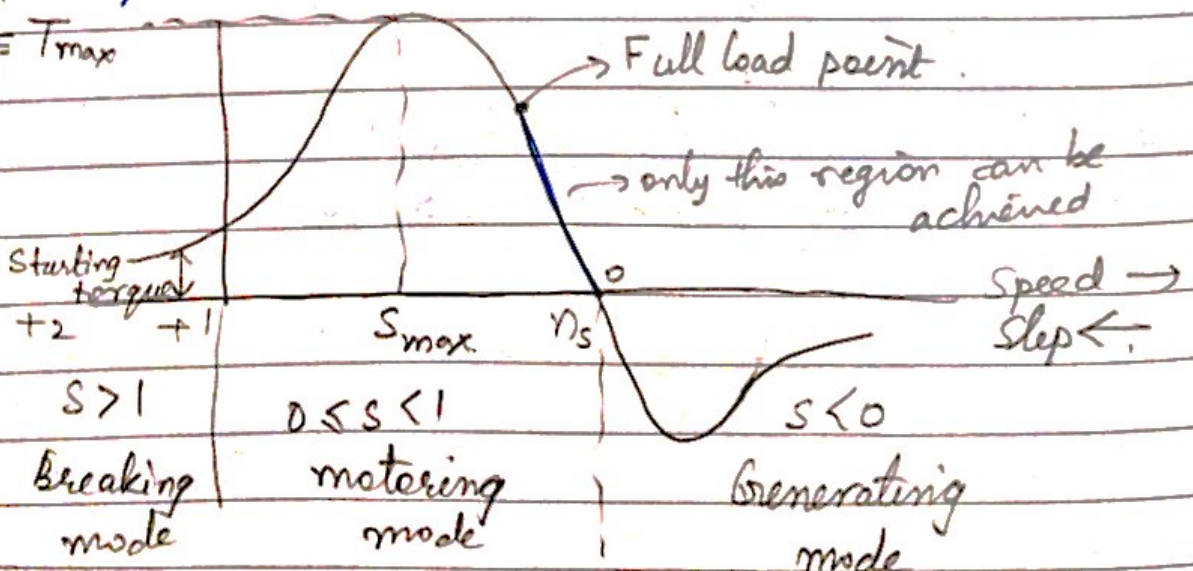

* Motoring mode

$0 < s < 1$: Subynchronous speed

* Breaking mode

$s > 1$: motor runs in opp. dirⁿ to field of stator.

* Generating mode:

$s < 0$: supersynchronous speed in dirⁿ of rotating field.


* WRIM

External resistance can be added to rotor - only possible in slip ring rotor. As R_2 is added,

(i) Breakdown torque (max torque) remains unchanged.

(ii) Slip at breakdown torque \uparrow

(iii) T_{start} becomes max.

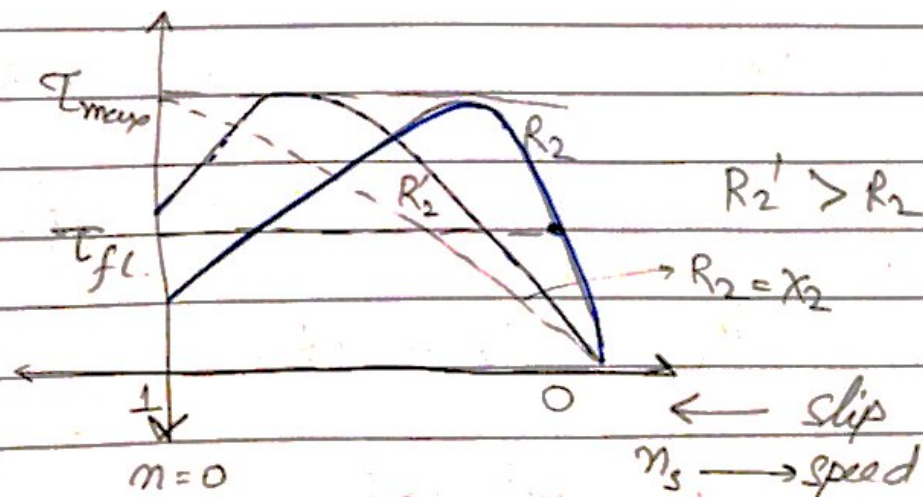

\Rightarrow As $R \uparrow$, s at $T_{max} \uparrow$.

Q. A 6-pole, 50 Hz, 3 ϕ IM running on f.l develops a useful torque of 160 N-m when rotor emf makes 120 complete ~~or~~ cycles/min. Calculate shaft power o/p. If mech. torque lost in friction & that for core loss is 10 N-m, find

(a) Cu loss in motor (b) o/p to motor (c) η

Ans Here, Total stator loss = 800 W

$$\text{frequency of rotor emf, } f_2 = \frac{120}{60} = 2 \text{ Hz (given)} = 5f$$

$$\text{slip} = \frac{2}{50} = 0.04 = 4\%$$

$$n_s = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$n = \text{rotor speed} = (1-s) \times n_s = (1-0.04) \times 1000 = 960 \text{ rpm}$$

$$\omega = \frac{2\pi n}{60} = \frac{2\pi \times 960}{60} = 100.53 \text{ rad/sec}$$

$$\text{Shaft power o/p} = T \cdot \omega = 160 \times 100.53 = 16.085 \text{ kW}$$

$$\text{Mechanical power developed } \left\{ \begin{array}{l} P_m = (\text{useful } T + T_{\text{in rot. loss}}) \times \omega \\ = (160 + 10) \times 100.53 \\ = 17.09 \text{ kW} \end{array} \right.$$

$$(a) P_m = 3(I_2')^2 R_2' \left(\frac{1}{s} - 1 \right)$$

$$\text{Rotor Cu loss} = 3(I_2')^2 R_2' = P_m \left(\frac{s}{1-s} \right) = 712 \text{ W}$$

$$\text{Net salary} = \text{Gross Salary} + \text{Deduction}$$

|||
Loss

(b) Motor i/p = $P_m + \text{Rotor Cu loss} + \text{Total stator loss}$
 $= 17.09 + 0.712 + 0.8 = 18.602 \text{ kW}$

(c) $\eta = \frac{\text{Shaft power of motor i/p}}{\text{Total i/p}}$
 $= \frac{16.085}{18.602} = 86\%$

Q A 40 kW, 440 V, 3 ϕ , 50 Hz, 8 pole squirrel cage rotor IM has a slip of 0.03 when operated at rated voltage & frequency. If full load line current is 68.9 A & efficiency 89.6%, find
 (a) shaft T delivered to load.
 (b) pf at which motor operates.

$$\eta = \frac{\text{O/P}}{\text{I/P}} = 89.6 \Rightarrow \text{O/P} = \frac{89.6 \times 40}{100} = 35.84 \text{ kW}$$

Now, O/P power = $T_{sh} \times \omega$

$$\Rightarrow T_{sh} = \frac{35.84 \times 60}{2\pi \times 750} \rightarrow \text{D}$$

Now, $n_s = \frac{120f}{P} = \frac{120 \times 50}{8} = 750 \text{ rpm}$

Now, $S = 0.03 = \frac{n_s - n}{n_s}$

$$\Rightarrow n = n_s (1 - 0.03)$$

$$\Rightarrow n = 750 (0.97) = 727.5 \text{ rpm}$$

* Note: Find slip (s) or n (rotor speed) in any problem of IM

$$\Rightarrow T_{sh} = \frac{3584}{2\pi \times 727.5} \times 60$$

$$= 0.47 \text{ kNm}$$

$$\Rightarrow T_{sh} = 470 \text{ Nm}$$

(b) Motor $\frac{1}{p} = \sqrt{3} V_L I_L \cos \phi$
 $= \sqrt{3} \times 440 \times 68.9 \times \cos \phi$
 40 kw \Rightarrow pf = 0.7617

* Normally, IM has a lagging pf.

Imp *
Learn

Torque & Slip characteristics.

$$T \propto E_r I_r \cos \phi_2 \quad \text{or} \quad T \propto \phi I_r \cos \phi_2$$

for rotor
for standstill
(since $E_r \propto \phi$)

E_r : rotor emf/phase under running condⁿ

I_r : rotor current/phase " " "


$E_r = s E_2$ where E_2 : standstill rotor induced emf/phase

$$I_r = \frac{E_r}{Z_r} = \frac{s E_2}{\sqrt{R_2^2 + (s X_2)^2}}$$

R_2 : rotor resistance

X_2 : standstill rotor reactance/phase
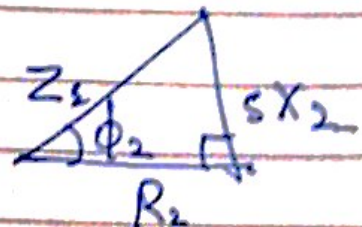
$$\cos \phi_2 = \frac{R_2}{\sqrt{R_2^2 + (s X_2)^2}}$$



$$T \propto \phi \cdot \frac{s E_2}{\sqrt{R_2^2 + (s X_2)^2}} \cdot \frac{R_2}{\sqrt{R_2^2 + (s X_2)^2}} = \frac{k \phi s E_2 R_2}{R_2^2 + (s X_2)^2} \rightarrow \text{A}$$

$$T_s = \frac{k_1 s E_2^2 R_2}{R_2^2 + (s X_2)^2}, \text{ since } E_2 \propto \phi.$$

For T_s , put $s = 1$

$$\text{At standstill, } s = 1, T_{\text{starting}} = T_s = \frac{k_1 E_2^2 R_2}{R_2^2 + X_2^2}$$

$$\text{If } V \text{ is const, } \frac{dT_s}{dR_2} = 0.$$

$$\Rightarrow \frac{dT_s}{dR_2} = k_1 \left[\frac{1}{R_2^2 + X_2^2} - \frac{R_2 (2R_2)}{(R_2^2 + X_2^2)^2} \right] = 0$$

$$\Rightarrow R_2 = X_2 \text{ : cond}^n \text{ for max starting torque.}$$

Starting torque of squirrel cage motor.

↳ rotor resistance can't be changed

$$\text{Starting torque} = 1.5 \times T_{fl}$$

$$\text{Starting current} = 5 \text{ to } 7 \times I_{fl}$$

$$\frac{dT_s}{dR_2} = 0$$

$$dR_2$$

$$\text{Proof } \Rightarrow \frac{(R_2^2 + X_2^2)(k_1 E_2^2) - k_1 E_2^2 R_2 (2R_2)}{(R_2^2 + X_2^2)^2}$$

$$= k_1 \left[\frac{E_2^2}{R_2^2 + X_2^2} - \frac{2E_2^2 R_2}{(R_2^2 + X_2^2)^2} \right] = 0$$

$$\Rightarrow R_2^2 + X_2^2 = 2R_2^2$$

$$\Rightarrow R_2 = X_2, \checkmark$$

• Condⁿ for max. torque \rightarrow differentiating τ expression w.r.t s & equate to zero!

From (A)

$$\frac{d\tau}{ds} \cdot \frac{[R_2^2 + (sX_2)^2][E_2 R_2 k\phi] - (k\phi E_2 R_2 s)(2sX_2)}{(R_2^2 + (sX_2)^2)^2} = 0$$

$$= 0$$

$$\Rightarrow 2s^2 X_2^2 = R_2^2 + s^2 X_2^2$$

$$\Rightarrow \boxed{R_2 = sX_2}$$

For max. τ : substitute $R_2 = sX_2$ in (A)

$$\begin{aligned} \Rightarrow \tau_{\max} &= \frac{k\phi s E_2 (sX_2)}{(sX_2)^2 + (sX_2)^2} \\ &= \frac{k\phi s E_2}{2sX_2} \end{aligned}$$

$$\Rightarrow \boxed{\tau_{\max} = \frac{k\phi E_2}{2X_2}}$$

★ Effect of change in supply voltage V on torque:
 $E_2 \propto \phi \propto V$.

$$\text{So, } \tau = \frac{k\phi s E_2 R_2}{R_2^2 + (sX_2)^2} \propto V^2.$$

So, T is very sensitive to change in V .

* Full load T & T_{max} :- $\frac{T_f}{T_{max}} = \frac{2as_f}{a^2 + s_f^2} \rightarrow (1)$

f' \rightarrow s_f : slip corresponding to f.l. torque.

* Starting torque & T_{max} $\frac{T_{s}}{T_{max}} = \frac{2a}{1+a^2} \rightarrow (2)$

Starting $\rightarrow a = \frac{R_2}{X_2}$

Proof
of
eqⁿ (1)

$$T_f = \frac{k\phi s_f E_2 R_2}{R_2^2 + (s_f X_2)^2}$$

$$T_{max} = \frac{k\phi s E_2 (s X_2)}{(s X_2)^2 + (s X_2)^2}$$

$$T_{max} = \frac{k\phi E_2}{2 X_2}$$

$$\Rightarrow \frac{T_f}{T_{max}} = \frac{k\phi s_f E_2 R_2}{R_2^2 + (s_f X_2)^2} \times \frac{2 X_2}{k\phi E_2}$$

$$\Rightarrow \frac{2 s_f X_2 R_2}{\left[\left(\frac{R_2}{s_f X_2} \right)^2 + 1 \right] (s_f X_2)^2}$$

$$= \frac{2 R_2}{\left(\frac{a^2 + 1}{s_f^2} \right) s_f X_2}$$

$$= \frac{2 s_f R_2}{(a^2 + s_f^2) s_f X_2} = \frac{2as_f}{(a^2 + s_f^2)}$$

$$= \frac{2as_f}{(a^2 + s_f^2)}$$

Q A 4 pole 50 Hz 3 ϕ IM has rotor resistance per phase $(R_2/\phi) = 0.03 \Omega$, $X_2 = 0.12 \Omega/\phi$.

→ Rotor standstill reactance

- ✓ What is speed at T_{max} ?
- ✓ Find amt. of $R_{external}/\phi$ to be inserted to get 75% of T_{max} at start?

(S1) Find synchronous speed

↳ needed to find rotor speed

$$n_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

Note \leftarrow For $T_{max} \Rightarrow R_2 = sX_2$

$$\Rightarrow (R_2/\phi) = s(X_2/\phi)$$

$$\Rightarrow s = \frac{0.03}{0.12}$$

$$\Rightarrow s = 0.25$$

Now, $n_s \checkmark$

$$\Rightarrow (n) \checkmark$$

→ rotor speed =

$$0.25 = n_s - n$$

$$\Rightarrow n = (1-s)n_s$$

$$= 1125 \text{ rpm}$$

$$T_{\text{reqd at start}} = (0.75) T_{\text{max}}$$

$$\Rightarrow \frac{T_c}{T_{\text{max}}} = 0.75 = \frac{2a}{1+a^2}$$

$$a = \frac{R_2}{X_2} = \frac{R_2}{0.12}$$

$$\Rightarrow 0.75 = 2 \left(\frac{R_2}{0.12} \right)$$

$$1 + \left(\frac{R_2}{0.12} \right)^2$$

$$\Rightarrow 0.75 \times 0.12 = \frac{2 R_2}{(0.12)^2 + R_2^2}$$

$$\Rightarrow (0.75 \times 0.12 \times 0.0144) + \frac{900 R_2^2}{10000} = 2 R_2$$

Time
Consuming

$$\Rightarrow \frac{1296}{1000000} + \frac{900 R_2^2}{10000} = 2 R_2$$

$$0.75 = \frac{2a}{1+a^2}$$

$$\Rightarrow a = 0.451 \Omega$$

(large value)
neglected

$$\text{Now, } a = \frac{R_2 + R}{X_2}$$

what
is asked.

(external R/φ to be added to rotor)

$$\Rightarrow R = 0.024 \Omega$$

Can be used.

* T_{max} : also called PULL OUT torque or Breakdown torque.

Q, A 50 Hz & pole IM has $X_f = 0.04$, $R_2 = 0.001 \Omega$ per phase & standstill reactance = $0.005 \Omega/\phi$.

(I) Find $T_{max}/f.l.$ & speed at which T_{max} occurs.

(II) A 3 ϕ IM has starting $T_s = 100\%$ of $T_f.l.$ &

$T_{max} = 200\%$ of $T_f.l.$
Find (a) slip at T_{max}
(b) f.l. slip.

(I) Just like previous ques.

$$(II) \frac{T_f}{T_{max}} = \frac{2as}{a^2 + s^2} \rightarrow (1)$$

$$\frac{T_s}{T_{max}} = \frac{2a}{1+a^2} \rightarrow (2)$$

Now, $T_s = T_f$ & $T_{max} = 2T_f$.

$$\Rightarrow \frac{T_{max}}{T_s} = 2 \rightarrow (3)$$

$$\text{By, } \frac{T_s}{T_{max}} = \frac{1}{2} \left(\because T_f = T_s \right)$$

$$\Rightarrow s_{\text{at } T_{\text{max}}} = 0.04$$

(a) solve for s_f using (1) & (2) & (3),

(b) we know $a = \frac{R_2}{X_2}$. At T_{max} $R_2 = s X_2$

$$\Rightarrow s = \frac{R_2}{X_2}$$

at T_{max}

★ Max. torque can also be measured in a unit Synchronous watts.

Q.2 & 9.5 P_{G1} : motor i/p - stator Cu loss -

A 3 ϕ 440V, 50 Hz 4 pole Y connected IM has $R_2 = 0.1 \Omega/\text{ph}$ & $X_2 = 0.9 \Omega/\phi$. Ratio of stator to rotor turns is 3.5. Calculate :-

- Gross op at a slip of 5%
- Max. torque in syn. watts & corresponding slip.

$$E_1 = \text{Stator phase voltage} = \frac{V_L}{\sqrt{3}} = \frac{440}{\sqrt{3}}$$

$$a = \frac{\text{Stator turns}}{\text{Rotor turns}} = 3.5 \text{ (given)}$$

$$\frac{E_1}{E_2} = \frac{n_1}{n_2} \quad (E \propto n)$$

$$\Rightarrow a = \frac{E_1}{E_2} = 3.5$$

$$\Rightarrow E_2 = \text{Standstill rotor emf } \phi = \frac{E_1}{3.5} = 72.6 \text{ V}$$

(transformⁿ req^d)

$$\Rightarrow E_r = \text{rotor emf} = s E_2 = 0.05 \times 72.6 = 3.63 \text{ V}$$

$$Z_2 = \sqrt{R_2^2 + (sX_2)^2} = 0.109 \Omega$$

$$I_2 = \frac{E_r}{Z_2} = 33.1 \text{ A}$$

$$\begin{aligned} \text{Rotor Cu Loss} &= 3 I_2^2 R_2 \text{ (derived before)} \\ &= 3 \times (33.1)^2 \times 0.1 \\ &\approx 330 \text{ W} \end{aligned}$$

We know,

$$\text{Power across air gap, } P_{G1} = \frac{\text{Rotor Cu Loss}}{\text{Slip}}$$

$$\begin{aligned}
 \Delta P_{\text{in}} = \text{Gross o/p} &= \frac{(1-s) P_g}{1} \\
 &= \frac{1-s}{s} \times \text{Rotor Cu loss} \\
 &= \frac{1-0.05}{0.05} \times 330 \\
 &= 19 \times 330 \\
 &= 6270 \text{ W}
 \end{aligned}$$

(b) At T_{max}

$$s = \frac{R_2}{X_2} = \frac{0.1}{0.9} = 0.11$$

$$\Rightarrow E_r = s E_2 = 0.11 \times 72.6 = 8.07 \text{ V}$$

(transformed again)
(due to slip change)

$$\text{Now, } Z_2 = \sqrt{R_2^2 + (s X_2)^2} = 0.1407 \Omega$$

$$I_2 = \frac{E_r}{Z_2} = 57.1 \text{ A}$$

$$\text{Rotor Cu loss} = 3 I_2^2 R_2 = 978.123$$

$$\begin{aligned}
 * P_{\text{in}} &= \frac{\text{Rotor Cu Loss}}{s_{\text{TM}}} = T_{\text{max}} \text{ in syn. watts} \\
 &= 8892.02 = T_{\text{max}} \text{ in syn. watts.}
 \end{aligned}$$

$$* T_G = \text{Gross torque} = \frac{P_m}{2\pi N/60} \quad ; N = N_s(1-s)$$

$$* \text{Speed at } T_{\text{max}} = (1-s_m) N_s \quad ; s_m = R_2/X_2$$

$$* \text{Gross torque} = \frac{P_m}{2\pi N/60} = \frac{P_{\text{in}}}{2\pi N_s/60}$$

* For induction machine, Induction motor is always used & Indⁿ generator is seldom used.

Puffin

Date _____

Page _____

* Indⁿ machine

Ch - Synchronous Machines

advantages:

It is

single fed.

* Sync. machines

2 supplies :-

AC to

Stator &

DC to

rotor

↓

to create

permanent

magnet

windings are distributed

basic structure

* Stator is similar to induction machine, wound for 3 ϕ . In sync. machine, rotor is excited with DC winding.

Synchronous machine

Sync. Generator (or Alternator)

Sync. Motor (Seldom used)

Diff rotor types :-

- Salient pole or Projecting pole type rotor
- Non-salient pole type rotor (or cylindrical rotor)

* Rotor Types

Cylindrical Rotor (Non-salient pole)

* Cylindrical form with DC field winding distributed

Projecting Pole type (Salient pole)

* Field winding concentrated

* Indⁿ motor

rotor speed $< \omega_{sync}$

Indⁿ generator

rotor speed $> \omega_{sync}$

Puffin

Date

Page

Non Salient

Salient

- high speed turbo alternators (≈ 20 MW power to be generated)
- Long rotor with small diameter
- 2 or 4 pole machine types
- Has uniform air gap
- low speed generators & sync. motors
- Large diameter with small length rotor
- Large no. of poles

* Synchronous machine \Rightarrow rotor runs at $\omega_s (= \frac{120f}{P})$ for production of torque - spring like synchronous link i.e. stator & rotor field

* rotor field & the stator field run at ω_s
So, they are stationary relative to each other

* Circuit models of synchronous machines
✓ with X_L (leakage reactance) neglected
✓ including X_L

* Due to armature reaction, $\sin \phi$

DC machines	Synchronous machines
cross magnetising	cross magnetising
demagnetising	demagnetising
	magnetising

* $X_s = \text{synchronous reactance}$
 $= X_a + X_l$
→ armature → leakage

* E_r : emf under loaded condⁿ
 ↳ called as: AIR GAP Emf.

* Ily as in DC machine, here, we have


Generating mode	Motoring Mode
$V_t = E_f - j X_s \bar{I}_a$	$V_t = E_f + j X_s \bar{I}_a$
	(I_a flows into mach)

* Z_s : synchronous impedance
 $= \text{Total impedance/phase}$
 $= \sqrt{R_a^2 + X_s^2}$

* Determination of X_s
 ↳ OC & SC Tests.

* OC

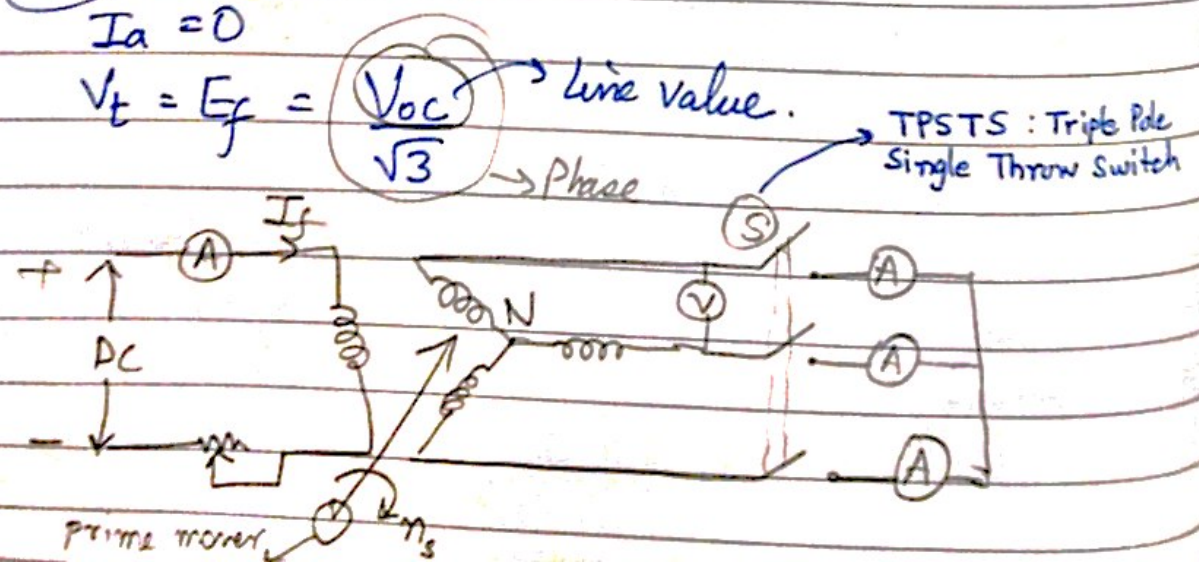$I_a = 0$
 $V_t = E_f = \frac{V_{oc}}{\sqrt{3}}$
→ line value. → Phase



OCC: Open circuit characteristics :- V_{oc} vs I_f .

* (SC) S: switch is closed.
Low I_f circulates.

$$\Rightarrow X_s (\text{unsaturated}) = \frac{V_{oc} \sqrt{3}}{I_{sc}} \quad \Bigg| \quad I_f : \text{const.}$$

SCC: I_{sc} vs I_f : linear: for low I_f
: unsaturated magnetic circuit.
= one pt. enough to plot graph

* OCC graph.

DC machine: has residual voltage
Synchronous: no residual voltage

* Under Loading cond^{ns}:-

$X_s (\text{adjusted}) < X_s (\text{unsaturated})$
(for a saturated magnetic circuit)

$$* X_s (\text{adjusted}) = \frac{V_{oc} \sqrt{3}}{I_{sc}} \quad \Bigg| \quad I_f \text{ corresponding to } V_t (\text{rated}) \text{ on OCC.}$$

$$* \text{Voltage regulation} = \frac{V_t (\text{no load}) \Big|_{I_f \text{ same as at full load}} - V_t (\text{rated})}{V_t (\text{rated})}$$

at specified pt

★ On air gap line \rightarrow unsaturated
 On OCC line \rightarrow adjusted

Q. Given: OCC & SCC data


Find: (a) unsaturated X_s

(b) adjusted X_s

(c) excitation voltage needed to give rated voltage at full load, 0.8 pf lagging. Use unsaturated X_s .

(d) Voltage regulation above load

General format

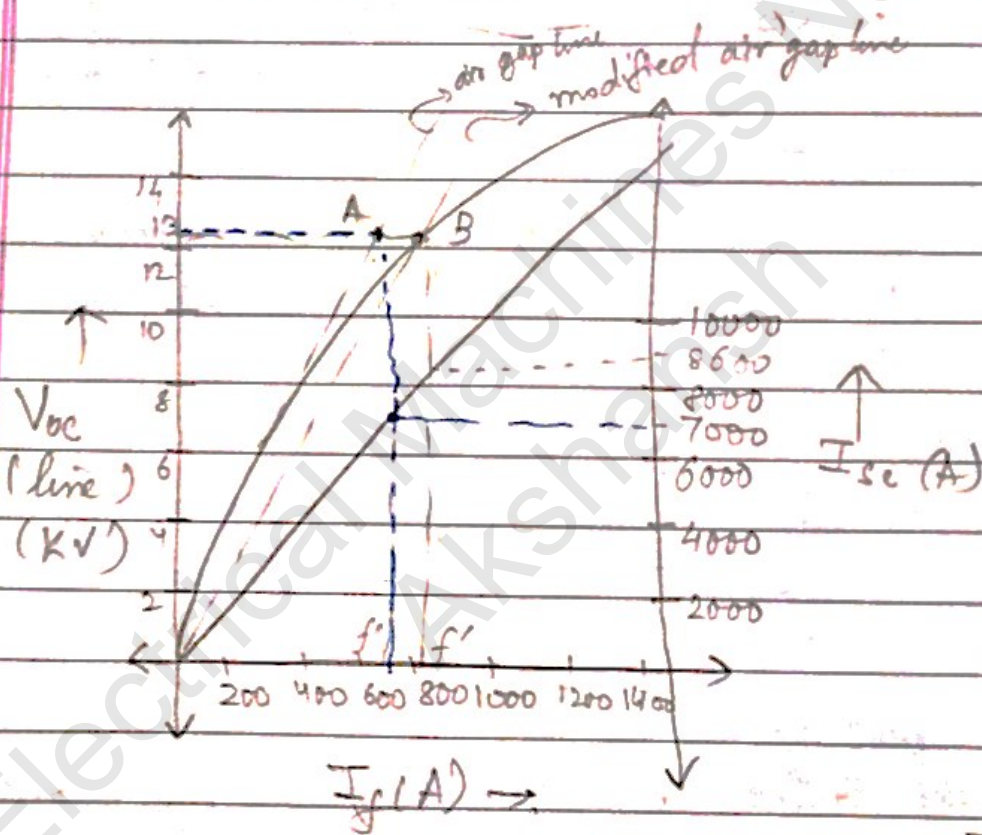

(a)
 pt. A X_s (unsaturated) = $\frac{(13 \times 10^3) / \sqrt{3}}{7000} = \frac{V_{oc} / \sqrt{3}}{I_{sc}}$
 $= 1.072 \Omega$

(b)
 pt. B X_s (adjusted) = $\frac{(13 \times 10^3) / \sqrt{3}}{8600} = 0.873 \Omega$

Clearly, X_s (adj) $<$ X_s (unsat.)

★ Synchronous generator: Also called Alternator

(c) Excitⁿ voltage to be found
 Always we require 2 things
 ✓ load
 ✓ V pf

$$V_t = \frac{(13 \times 10^3)}{\sqrt{3}} = 7505 \text{ V (phase value)}$$

$$V_t = 7505 \angle 0^\circ \text{ V}$$

$$\cos \phi = 0.8 \Rightarrow \phi = 36.9^\circ$$

$$I_a (fL) = \frac{\text{Power (rated)}}{\sqrt{3} \text{ Voltage}} \left(\begin{array}{l} \text{VA} \\ \rightarrow 13 \times 10^3 \end{array} \right)$$

$$\left(\because \text{Power} = \sqrt{3} V_L I_L \right. \\ \left. \text{or } 3 V_{ph} I_{ph} \right)$$

$$\Rightarrow I_a = 7837 \text{ A}$$

$$\Rightarrow \underline{I_a} = 7837 \angle -36.9^\circ \\ = 7837 (0.8 - j0.6)$$

For generating operⁿ:-

$$\underline{E_g} = V_t + j I_a X_s \quad \text{(Phase value)}$$

Case (D):-

$$X_s (\text{unsat}) = 1.072 \Omega$$

$$E_g = 7505 + j(7837)(0.8 - j0.6) \times 1.072 \\ = 12546 + j6721$$

$$E_g = 14233 \text{ V or } (24.65 \text{ kV (line)}) \\ = V_L (OC) \text{ (linear mode)} \rightarrow 14233 \times \sqrt{3}$$

★ Diff. b/w Watt & VA (Volt Ampere)
 (VA) Power = $\sqrt{3} V_L I_L = 3 V_{ph} I_{ph}$
 (W) Power = $\sqrt{3} V_L I_L \cos \phi = 3 V_{ph} I_{ph} \cos \phi$

Puffin

Date: _____
 Page: _____

→ Pf comes into picture when P given in watts

(d) Regulⁿ :-
$$\frac{V_{t(OC)} - V_t}{V_t} \times 100$$

$$= \frac{14233 - 7505}{7505} \times 100 = 89.64\%$$

Note :- Voltage regulⁿ values :-

1-2% : Transformer

> 60% : Alternator

★ Purpose of sync. generator :- To generate a 3 ϕ AC voltage

★ Bulb experiment in lab

Bus Bar :- Sth. with which we connect alternator (generating voltage)

↓ feeds power to city
 constt I, V

★ Synchronizⁿ :- Process of above connection.

also called
Paralleling


also called
Bus bar

★ Synchronising to mains

- machine runs as generator - same phase sequence as mains

Its speed & field current are adjusted
l.t

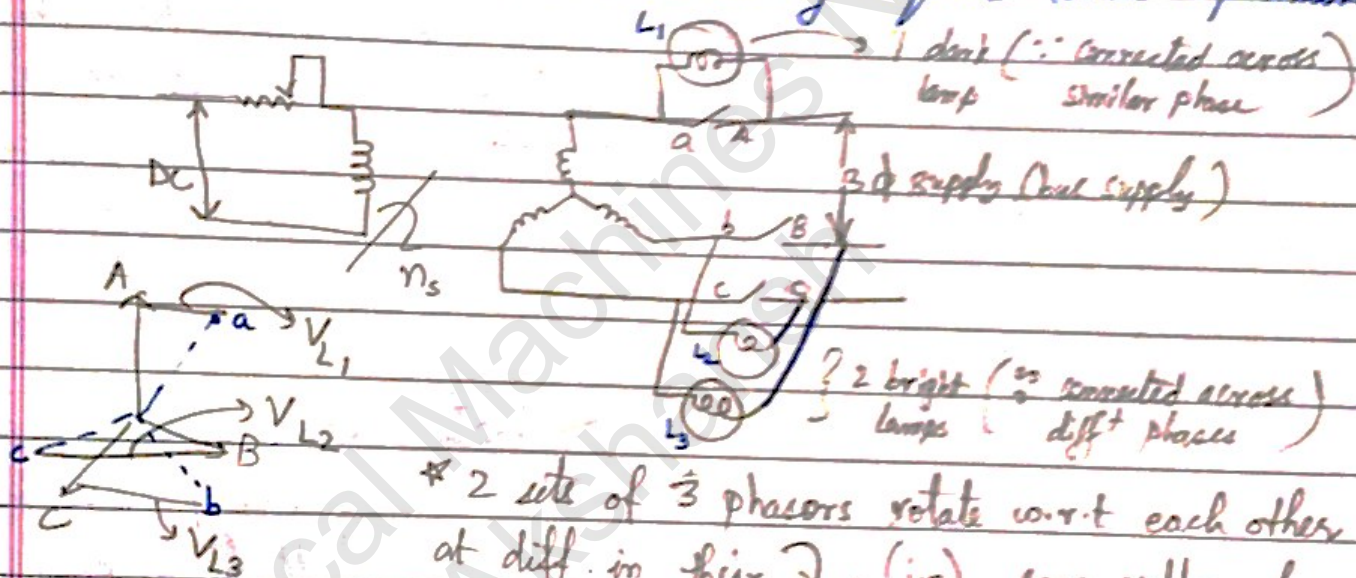- machine V_t nearly equals that of mains.
- machine \angle nearly equal that of mains



* 2 sets of 3 phasors rotate w.r.t each other at diff. in their \angle . (i.e.), rms voltage of 3 lamps rotate at diff \angle

- At instant of syne. action, 2 sets of phasors co-phased
 $V_{L1} = 0, V_{L2} = V_{L3}$ bright machine is switched on the mains
dark
- Instead of lamps, synchroscope is used
- Acceptable ϕ diff in phasor set is $\approx 5^\circ$
- DAMPER winding (or AMORTISSUR winding)
 - ↳ Oscill^{ns} due to synchronism
 - ↳ hunting - tackled by SC Cu bars in rotor pole faces
 - ↳ Indⁿ start synch. motor ——— LEARN

end of syllabus